

Given  $R = 100 \Omega$ ,  $C = 2 \mu F$ ,  $L = 80 m H$ ,  $V_s = 10 \cos(1256.637 t)$ , determine values of the following variables at AC steady state:

Q1. Magnitude of  $V_s$  in  $V_p$  (peak voltage), 10

Q2. Frequency of  $V_s$  in Hz, 200

Q3. Phase of  $V_s$  in radian within range  $(-\pi, \pi]$ , 0

Q4. Phasor  $V_s$  in rectangular form (if it is a complex, write in  $a + j b$  format---there is a space between  $j$  and the imaginary number),  $10 + j 0$

Q5. Impedance of resistor  $R$  in ohm, 100

Q6. Impedance of capacitor  $C$  in ohm (if it is a complex, write in  $a + j b$  format---there is a space between  $j$  and the imaginary number),

Q7. Impedance of inductor  $L$  in ohm (if it is a complex, write in  $a + j b$  format---there is a space between  $j$  and the imaginary number),

Q8. Magnitude of current  $i_R$  in A (peak ampere)

Q9. Frequency of current  $i_R$  in Hz,

Q10. Phase of current  $i_R$  (with reference to the phase of voltage  $V_s$ ) in radian within range  $(-\pi, \pi]$ .

*Hint: convert  $V_s$  to phasor and use phasor analysis.*


Write your answers in the following format.

Q1.1. magp\_vs = 0 V  
 Q1.2. freq\_vs = 0 Hz  
 Q1.3. phase\_vs = 0 rad  
 Q1.4. rec\_phasor\_vs = 0 V  
 Q1.5. ZR = 0 ohm  
 Q1.6. ZC = 0 ohm  
 Q1.7. ZL = 0 ohm  
 Q1.8. magp\_ir = 0 A  
 Q1.9. freq\_ir = 0 Hz  
 Q1.10. phase\_ir = 0 rad

$Z_C = \frac{2}{j\omega C}$   
 $Z_L = j\omega L$

$a + jb$   
 $R_c$   
 $I_m$

$$i = \frac{0V}{R}$$

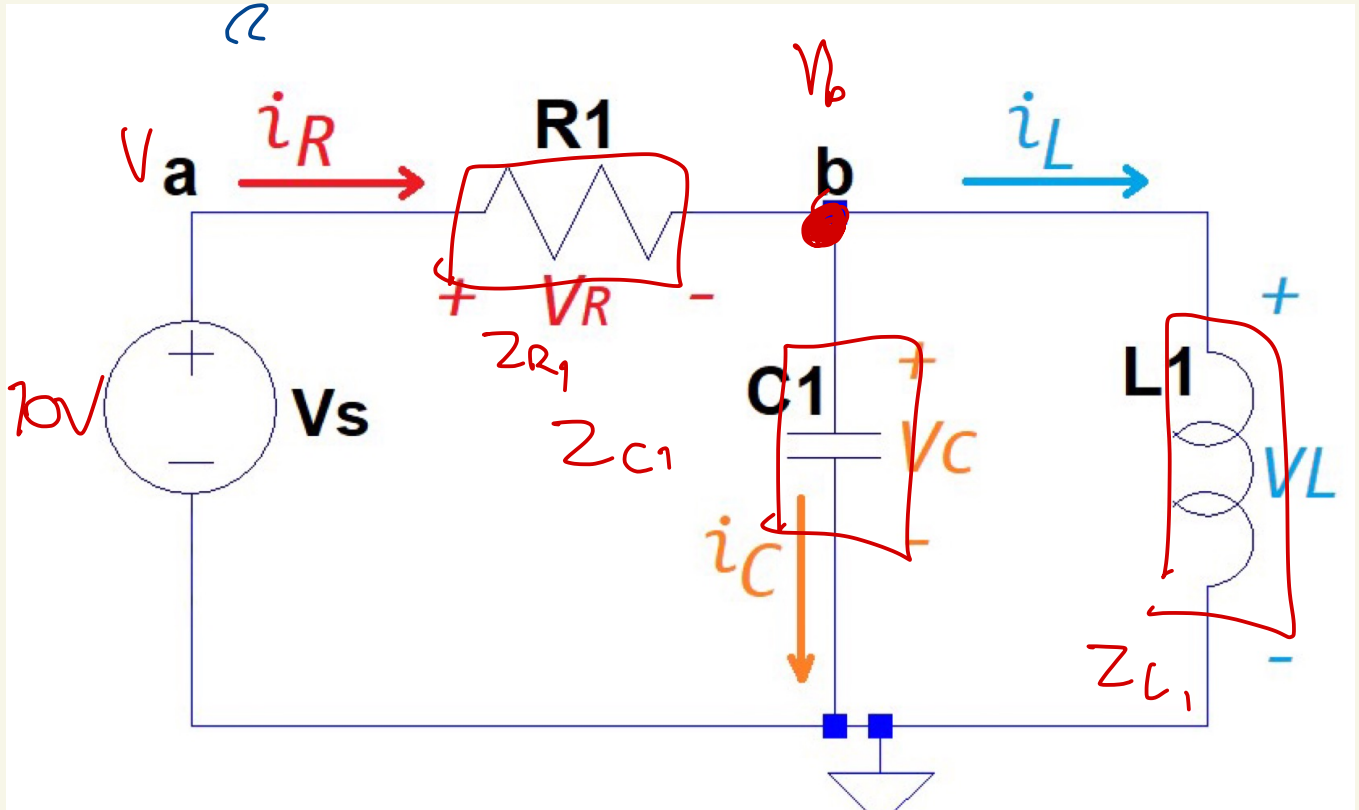

$$\frac{10 - V_b}{Z_R} + \frac{V_b}{Z_C} + \frac{V_b}{Z_L} = 0$$

$$\frac{10}{Z_R} - \frac{V_b}{Z_R} + \frac{V_b}{Z_C} + \frac{V_b}{Z_L} = 0$$

$$V_b \left( -\frac{1}{Z_R} + \frac{1}{Z_C} + \frac{1}{Z_L} \right) = -\frac{10}{Z_R}$$

$$V_b = \frac{-10}{Z_R} \div \left( -\frac{1}{Z_R} + \frac{1}{Z_C} + \frac{1}{Z_L} \right)$$

$$i_R = \frac{10 - V_b}{Z_R}$$