

# EN811100

# LINEAR CIRCUIT

# ANALYSIS

---

Chapter 2

Basic Laws

Dec 20, 2019

C. K. Alexander – M. N. O. Sadiku  
Fundamentals of Electric Circuits, 5<sup>th</sup> Edition, The McGraw-Hill Companies 2013  
J. A. Svoboda – R. C. Dorf  
Introduction to Electric Circuits, 9<sup>th</sup> edition, John Wiley & Sons, Inc. 2014 <sub>1</sub>

## Basic Laws - Chapter 2


- 2.1 Ohm's Law.
- 2.2 Nodes, Branches, and Loops.
- 2.3 Kirchhoff's Laws.
- 2.4 Series Resistors and Voltage Division.
- 2.5 Parallel Resistors and Current Division.
- 2.6 Voltmeters and Ammeters.
- 2.7 Multimeters.

## 2.1 Ohms Law

- Ohm's law states that the voltage across a resistor is directly proportional to the current  $I$  flowing through the resistor.
- Mathematical expression for Ohm's Law is as follows:

$$v = iR$$

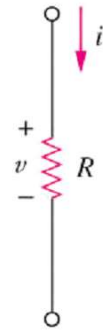- Two extreme possible values of  $R$ : **0 (zero)** and  **$\infty$  (infinite)** are related with two basic circuit concepts: **short circuit** and **open circuit**.



3


### Historical

**Georg Simon Ohm** (1787–1854), a German physicist, in 1826 experimentally determined the most basic law relating voltage and current for a resistor. Ohm's work was initially denied by critics.

Born of humble beginnings in Erlangen, Bavaria, Ohm threw himself into electrical research. His efforts resulted in his famous law. He was awarded the Copley Medal in 1841 by the Royal Society of London. In 1849, he was given the Professor of Physics chair by the University of Munich. To honor him, the unit of resistance was named the ohm.



© SSPL via Getty Images

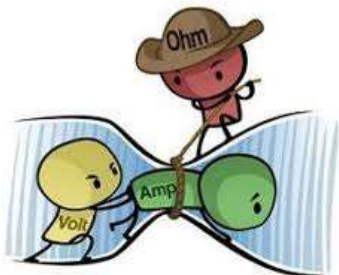


$$V = IR$$

4

## 2.1 Ohms Law
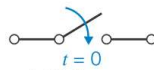
### Switches

Switches have two distinct states: open and closed. Ideally, a switch acts as a short circuit when it is closed and as an open circuit when it is open.




Initially open



Initially closed



Break before make

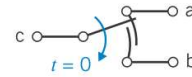

Make before break

### SPST Switches



Single Pole Single Throw


### SPDT Switches



Single Pole Dual Throws


## 2.1 Ohms Law

### Example a circuit with switches

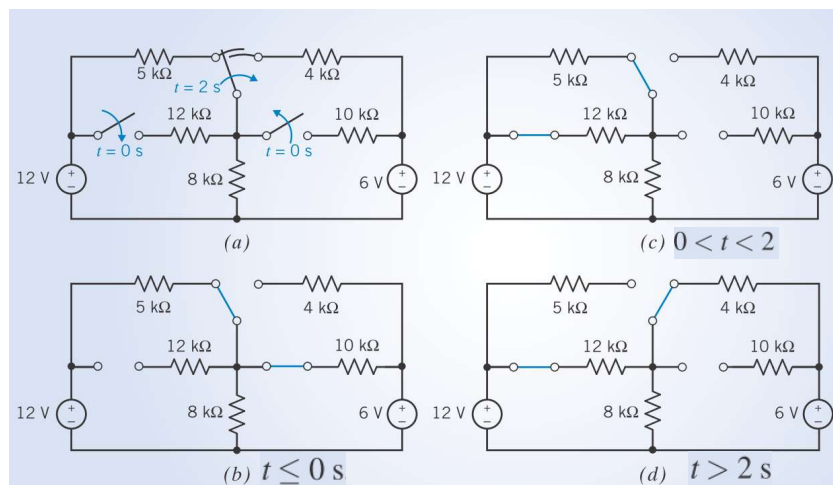


## 2.1 Ohms Law

The i-v characteristic of

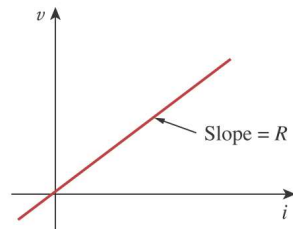

a linear resistor

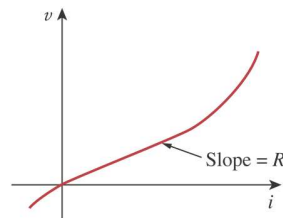


a nonlinear resistor

In this course, all the elements that are designated as resistors are linear (unless mentioned otherwise).

7

## 2.1 Ohms Law

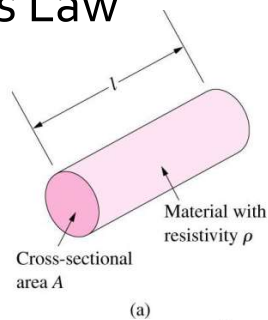

$$R \propto \frac{l}{A}$$

(Unit of  $\rho$  = Ohm-meter)

The constant of the proportionality is the resistivity of the material, i.e.,  $\rho$

$$R = \rho \frac{l}{A}$$

The *resistance*  $R$  of an element denotes its ability to resist the flow of electric current; it is measured in ohms ( $\Omega$ ).

8

## 2.1 Ohms Law

Resistivities of common materials.

Material	Resistivity ( $\Omega \cdot m$ )	Usage
Silver	$1.64 \times 10^{-8}$	Conductor
Copper	$1.72 \times 10^{-8}$	Conductor
Aluminum	$2.8 \times 10^{-8}$	Conductor
Gold	$2.45 \times 10^{-8}$	Conductor
Carbon	$4 \times 10^{-5}$	Semiconductor
Germanium	$47 \times 10^{-2}$	Semiconductor
Silicon	$6.4 \times 10^2$	Semiconductor
Paper	$10^{10}$	Insulator
Mica	$5 \times 10^{11}$	Insulator
Glass	$10^{12}$	Insulator
Teflon	$3 \times 10^{12}$	Insulator

9

## 2.1 Ohms Law

- Conductance is the ability of an element to conduct electric current; it is the reciprocal of resistance  $R$  and is measured in mhos or siemens.

$$G = \frac{1}{R} = \frac{i}{v}$$

**Conductance** is the ability of an element to conduct electric current; it is measured in mhos ( $\mathcal{U}$ ) or siemens (S).

- The power dissipated by a resistor:

$$p = vi = i^2 R = \frac{v^2}{R}$$


10

## Ohms Law Summary

$$V = IR$$

$$P = VI$$

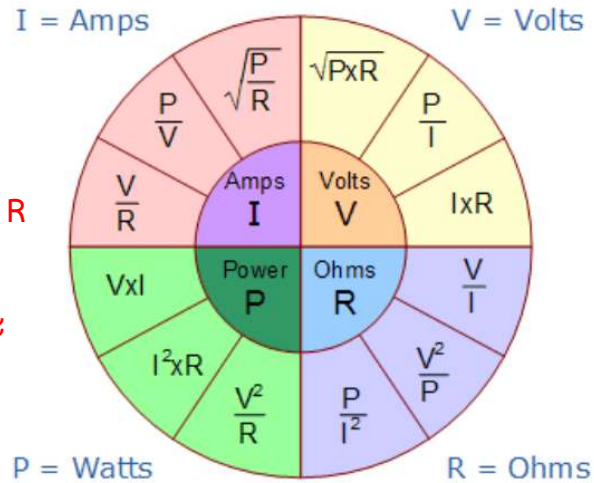
การหาค่า P, V, I, R  
ถ้าเราทราบ 2 ค่า  
อีก 2 ค่าที่เหลือจะ  
ตามมา



## 2.1 Ohms Law

### Fixed Resistors

- Inside the resistor

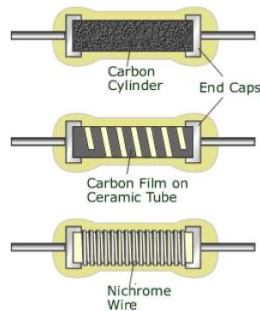

- A common type of resistor that you will work with in your labs:
- It has 4 color-coded bands (3 for value and one for tolerance)
  - How to read the value of the resistor?




12

## 2.1 Ohms Law
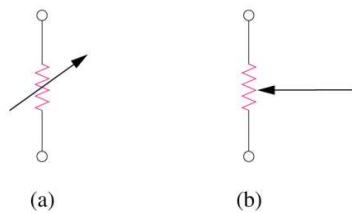
### Variable Resistors

- Variable resistors have adjustable resistance and are typically called potentiometer (or pot for short).
- Potentiometers have three terminals one of which is a sliding contact or wiper.



13

## 2.2 Nodes, Branches and Loops

- A **branch** represents a single element such as a voltage source or a resistor.
- A **node** is the point of connection between two or more branches.
- A **loop** is any closed path in a circuit.

Mesh



- A network with  $b$  branches,  $n$  nodes, and  $l$  independent loops will satisfy the fundamental theorem of network topology:

Independent loop

หมายถึง Loop ที่ประกอบด้วย

Branch อย่างน้อย 1 Branch

ที่ไม่เป็นของ Loop อื่น



$$b = l + n - 1$$

14

## 2.2 Nodes, Branches and Loops

Branch = 5, Loop = 3, Node = 3

### Example 1

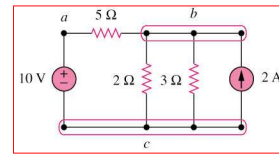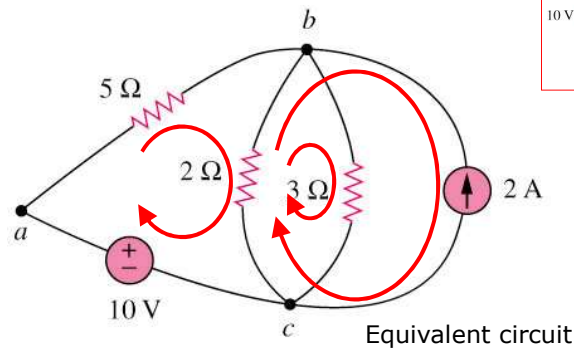

$$b = l + n - 1$$

$$5 = 3 + 3 - 1$$

How many branches, nodes and loops are there?

15

### Historical




© Pixallage Fotostock RF

**Gustav Robert Kirchhoff** (1824–1887), a German physicist, stated two basic laws in 1847 concerning the relationship between the currents and voltages in an electrical network. Kirchhoff's laws, along with Ohm's law, form the basis of circuit theory.

Born the son of a lawyer in Königsberg, East Prussia, Kirchhoff entered the University of Königsberg at age 18 and later became a lecturer in Berlin. His collaborative work in spectroscopy with German chemist Robert Bunsen led to the discovery of cesium in 1860 and rubidium in 1861. Kirchhoff was also credited with the Kirchhoff law of radiation. Thus Kirchhoff is famous among engineers, chemists, and physicists.


Kirchhoff Current Law  
(applied at node)

$$\sum_{n=1}^N i_n = 0$$

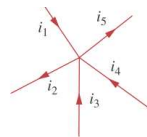

Kirchhoff Voltage Law  
(applied at loop)

$$\sum_{m=1}^M v_m = 0$$

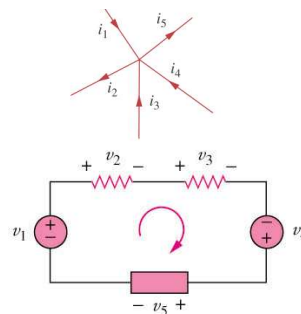



16



## 2.3 Kirchhoff's Laws

- Kirchhoff's current law (KCL) states that the algebraic sum of currents entering a node (or a closed boundary) is zero.

(มาจาก กฎการอนุรักษ์ประจุไฟฟ้า)

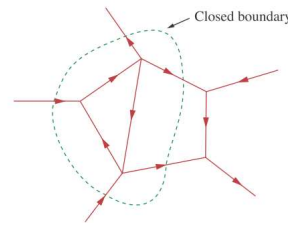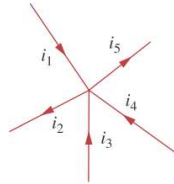

$$i_1 + (-i_2) + i_3 + i_4 + (-i_5) = 0 \rightarrow \text{กระแสรวมที่ Node} = 0$$


or

$$i_1 + i_3 + i_4 = i_2 + i_5 \rightarrow \text{กระแสที่เข้า} = \text{กระแสที่ออก}$$


Mathematically,  $\sum_{n=1}^N i_n = 0$  or  $\sum i_{IN} = \sum i_{OUT}$

17

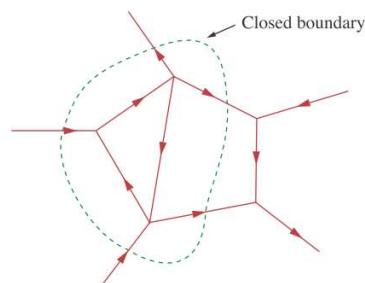- Kirchhoff's current law (KCL) states that the algebraic sum of currents entering a node (or a closed boundary) is zero.



=

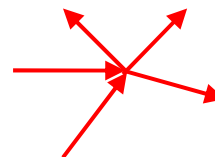

Closed boundary มองเป็น 1 Node ก็ได้

18

การกำหนดเครื่องหมาย + - ของกระแส

❖ ในกรณีที่เรานำสมการ

$$\sum_{n=1}^N i_n = 0$$


ให้กำหนดว่ากระแสไหลเข้า จะต้องมีการหมายตรงข้าม  
กับ กระแสที่ไหลออก เช่น

กระแสไหลเข้าเป็น +  
กระแสไหลออกเป็น -

หรือ

กระแสไหลเข้าเป็น -

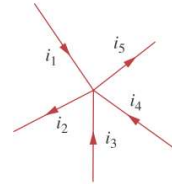กระแสไหลออกเป็น + (เลือกอย่างใดอย่างหนึ่ง)



$$i_1 + (-i_2) + i_3 + i_4 + (-i_5) = 0$$

การกำหนดเครื่องหมาย + - ของกระแส


❖ ในกรณีที่เรานำสมการ

$$\sum i_{IN} = \sum i_{OUT}$$

ให้จัดสมการให้กระแสไหลเข้าทั้งหมดอยู่ด้านหนึ่งของ  
สมการ

ส่วนอีกฝั่งหนึ่งของสมการ

ให้มีเฉพาะกระแสที่ไหลออก

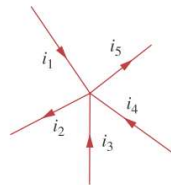


$$i_1 + i_3 + i_4 = i_2 + i_5$$

## 2.3 Kirchhoff's Laws
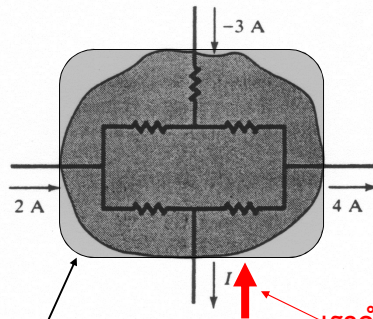
### Example 1

- Determine the current  $I$  for the circuit shown in the figure below.

ในตัวอย่างนี้กำหนดให้ กระแสไหลเข้าเป็น -, ไหลออกเป็น +



We can consider the whole enclosed area as one "node".

ไหลออก (+)      ไหลเข้า (-)

$$I + 4 - (-3) - 2 = 0$$

$$\Rightarrow I = -5A$$

This indicates that the actual current,  $I$  is flowing in the opposite direction.


เรากำหนดให้  $I$  ไหลออก แต่ถ้าเราได้คำตอบเป็นลบ แสดงว่าจริงๆ แล้ว  $I$  ไหลสวนทางกับที่เรากำหนด

21

## 2.3 Kirchhoff's Laws

- Kirchhoff's voltage law (KVL) states that the algebraic sum of all voltages around a closed path (or loop) is zero.

(มาจาก กฎการอนุรักษ์พลังงาน)

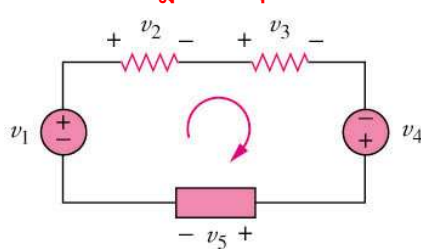

$$-v_1 + v_2 + v_3 - v_4 + v_5 = 0$$

Mathematically,

$$\sum_{m=1}^M v_n = 0$$

การกำหนดเครื่องหมาย + - ของแรงดัน

1. กำหนดทิศทางการไหลของกระแส

ภายใน Loop


2. ไล่ไปตามทิศทาง Loop ถ้าเราเจอ

ขั้วของแรงดันขั้วใดขึ้นก่อน จะได้

เครื่องหมายของแรงดันเป็นไปตามขั้วนั้น

22

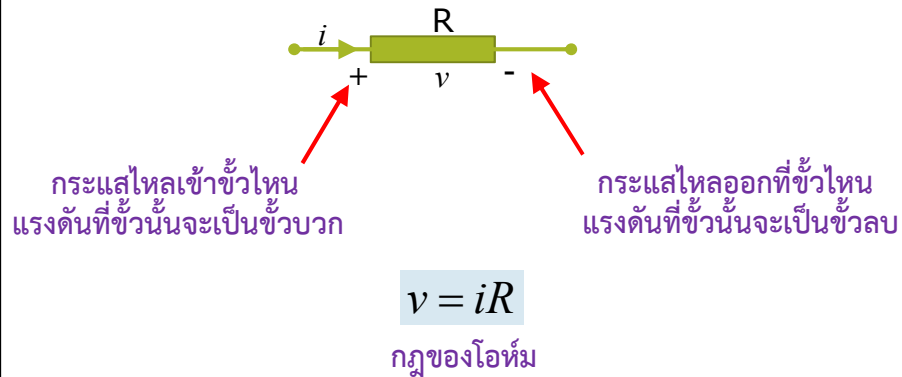การกำหนดค่าของแรงดันไฟฟ้าที่ตกคร่อมอุปกรณ์ไฟฟ้า  
ให้ดูจากทิศทางของกระแส



การกำหนดเครื่องหมายของแรงดันไฟฟ้าใน Loop

ให้ไล่วงจรตามทิศของกระแสใน Loop

ถ้าเจอแรงดันที่ขั้วลบขึ้นก่อน


แสดงว่า V ตัวนั้นจะมี


เครื่องหมายเป็นลบ

ถ้าเจอแรงดันที่ขั้วบวกขึ้นก่อน

แสดงว่า V ตัวนั้นจะมี

เครื่องหมายเป็นบวก

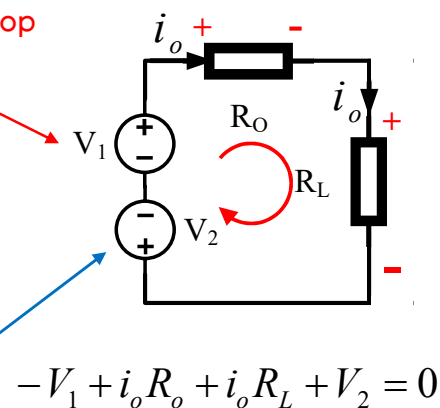

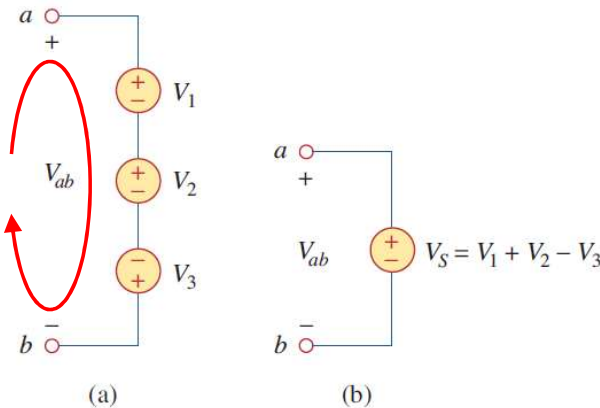

(a) (b)

$$V_1 + V_2 - V_3 - V_{ab} = 0$$

or


$$V_{ab} = V_1 + V_2 - V_3$$

25

## 2.3 Kirchhoff's Laws
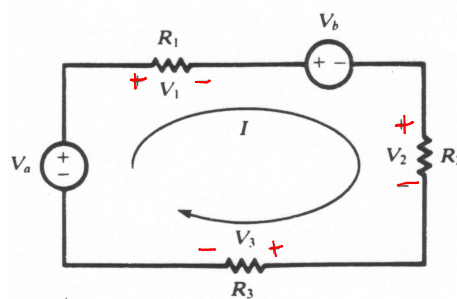
### Example 2

- Applying the KVL equation for the circuit of the figure below.



$$-v_a + v_1 + v_b + v_2 + v_3 = 0$$

$$v_1 = IR_1 \quad v_2 = IR_2 \quad v_3 = IR_3$$


$$\Rightarrow v_a - v_b = I(R_1 + R_2 + R_3)$$

$$I = \frac{v_a - v_b}{R_1 + R_2 + R_3}$$

## 2.3 Kirchhoff's Laws
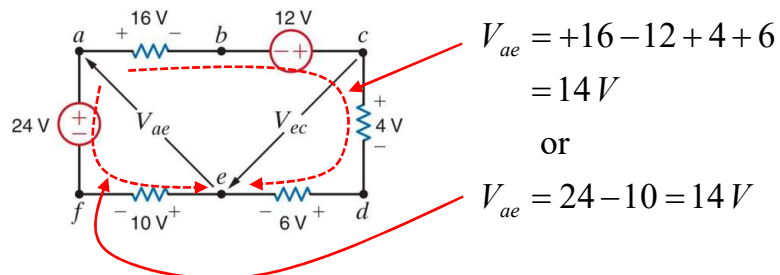
### Exercise

In the following circuit use KVL to determine  $V_{ae}$  and  $V_{ec}$ . Note that we use the convention  $V_{ae}$  to indicate the voltage of point a with respect to point e or  $V_{ae} = V_a - V_e$



$$V_{ec} = -6 - 4 = -10 \text{ V} \quad \text{or} \quad V_{ec} = 10 - 24 + 16 - 12 = -10 \text{ V}$$

27


## 2.4 Series Resistors and Voltage Division

- Series: Two or more elements are in series if they are cascaded or connected sequentially and consequently carry the same current.
- The equivalent resistance of any number of resistors connected in a series is the sum of the individual resistances.


$$R_{eq} = R_1 + R_2 + \dots + R_N = \sum_{n=1}^N R_n$$

- The voltage divider can be expressed as
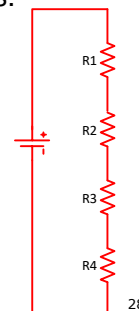
$$v_n = \frac{R_n}{R_1 + R_2 + \dots + R_N} v$$


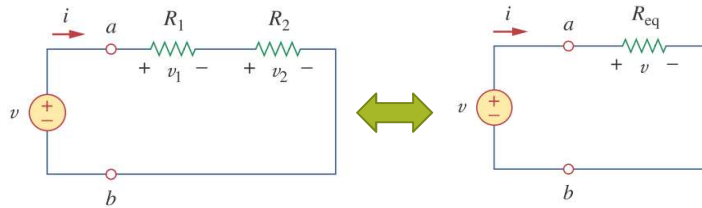
## 2.4 Series Resistors and Voltage Division (การแบ่งแรงดัน)



$$R_{eq} = R_1 + R_2 + \dots + R_N = \sum_{n=1}^N R_n \quad \Rightarrow \quad R_{eq} = R_1 + R_2 \quad \Rightarrow \quad i = \frac{v}{R_1 + R_2}$$

$$v_1 = \frac{R_1}{R_1 + R_2} v, \quad v_2 = \frac{R_2}{R_1 + R_2} v \quad \leftarrow \quad v = v_1 + v_2 = i(R_1 + R_2)$$

$$\Downarrow$$

$$v_n = \frac{R_n}{R_1 + R_2 + \dots + R_N} v$$

ใช้สำหรับหาแรงดันตกคร่อม  $R_n$  ในวงจร R ที่ต่ออนุกรมกัน

29


## 2.5 Parallel Resistors and Current Division

- Parallel: Two or more elements are in parallel if they are connected to the same two nodes and consequently have the same voltage across them.
- The equivalent resistance of a circuit with N resistors in parallel is:

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}$$

- The total current i is shared by the resistors in inverse proportion to their resistances. The current divider can be expressed as:

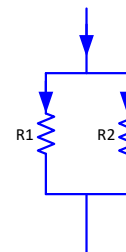
$$i_n = \frac{v}{R_n} = \frac{i R_{eq}}{R_n}$$



30

## 2.5 Parallel Resistors and Current Division

(การแบ่งกระแส)

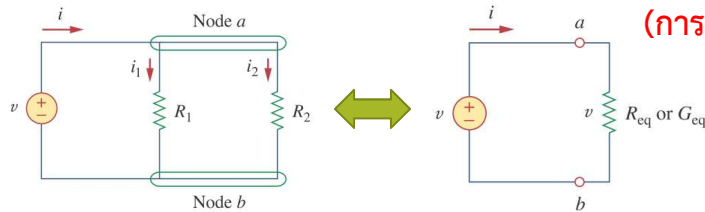

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N} \Rightarrow \frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} \Rightarrow i = \frac{v}{R_1} + \frac{v}{R_2} = v \left( \frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{v}{R_{eq}}$$

$$v = i_1 R_1 = i_2 R_2 \Rightarrow i_1 = \frac{v}{R_1}, \quad i_2 = \frac{v}{R_2} \quad v = \left( \frac{R_1 R_2}{R_1 + R_2} \right) i \quad i = v \left( \frac{R_1 + R_2}{R_1 R_2} \right)$$


ใช้คำนวณกระแส  
ที่ผ่าน  $R_n$  ในวงจร  
R ที่ต่อขนานกัน

$$i_1 = \frac{R_2 i}{R_1 + R_2}, \quad i_2 = \frac{R_1 i}{R_1 + R_2}$$

31

## 2.5 Parallel Resistors and Current Division

(การแบ่งกระแส)

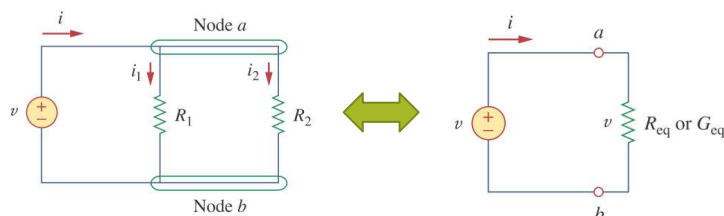

กรณีที่เราคำนวณโดยใช้ค่า Conductance (G)  $G = \frac{1}{R}$

สำหรับการต่อ R แบบขนานจะได้

$$G_{eq} = G_1 + G_2 + G_3 + \dots + G_N \quad \text{และ} \quad i_n = \frac{G_n}{G_1 + G_2 + \dots + G_N} i$$


$$i_1 = \frac{G_1}{G_1 + G_2} i \quad i_2 = \frac{G_2}{G_1 + G_2} i$$

32



## 2.5 Parallel Resistors and Current Division

### Example 3

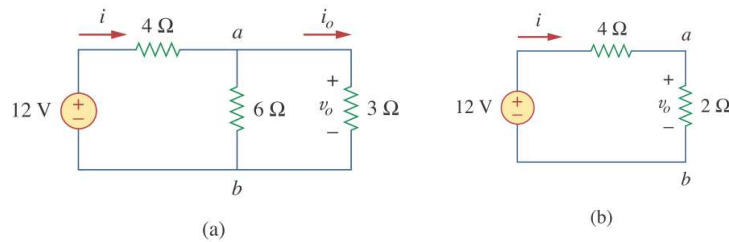

Find  $i_o$  and  $v_o$  and the power dissipated in the  $3\text{-}\Omega$  resistor

$$6\text{ }\Omega \parallel 3\text{ }\Omega = \frac{6 \times 3}{6 + 3} = 2\text{ }\Omega$$

$$\text{Apply Ohm's law } i = \frac{12}{4 + 2} = 2\text{ A}$$

33

## 2.5 Parallel Resistors and Current Division

$$v_o = 2i = 2 \times 2 = 4\text{ V}$$

Or apply voltage division

$$v_o = \frac{2}{2 + 4} (12\text{ V}) = 4\text{ V}$$

$$v_o = 3i_o = 4 \Rightarrow i_o = \frac{4}{3}\text{ A}$$

Or apply current division


$$i_o = \frac{6}{6 + 3} i = \frac{2}{3} (2\text{ A}) = \frac{4}{3}\text{ A}$$

The power dissipated in the  $3\text{-}\Omega$  resistor is

$$p_o = v_o i_o = 4 \left( \frac{4}{3} \right) = 5.333\text{ W}$$

34

## Summary

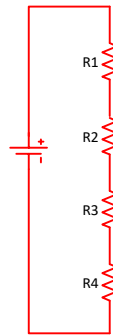


### Series resistors

$$R_{eq} = R_1 + R_2 + \cdots + R_N = \sum_{n=1}^N R_n$$
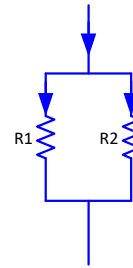
### Parallel resistors

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \cdots + \frac{1}{R_N}$$




35

### Practice Problem 2.9

By combining the resistors in Fig. 2.36, find  $R_{eq}$ .

Answer:  $10 \Omega$ .

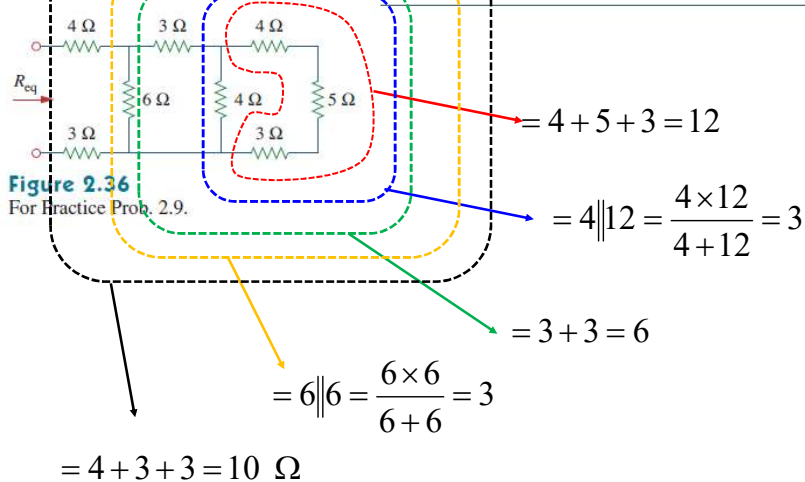


36

วิธีทำ
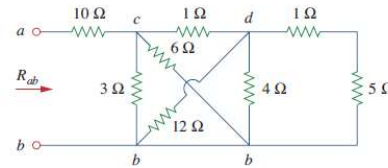
## Example 2.10

Calculate the equivalent resistance  $R_{ab}$  in the circuit in Fig.

$R = 1 \text{ Ohm}$   
 อนุกรมกับ  $5 \text{ Ohm} = 1 + 5 = 6$   
 $\downarrow$   
 ขนานกับ  $4 \text{ Ohm} = \frac{6 \times 4}{6 + 4} = 2.4$   
 $\downarrow$   
 ขนานกับ  $12 \text{ Ohm} = \frac{12 \times 2.4}{12 + 2.4} = 2$   
 $\downarrow$   
 อนุกรมกับ  $1 \text{ Ohm} = 2 + 1 = 3$   
 $\swarrow \quad \searrow$   
 ขนานกัน  $= \frac{2 \times 3}{2 + 3} = 1.2$   
 $\downarrow$   
 อนุกรมกับ  $10 \text{ Ohm} = 1.2 + 10 = 11.2 \text{ } \Omega$



Ans: 11.2 Ohms



$R = 3 \text{ Ohm}$  ขนานกับ  $6 \text{ Ohm}$   
 $= \frac{6 \times 3}{6 + 3} = 2$

$= \frac{2 \times 3}{2 + 3} = 1.2$

$\text{อนุกรมกับ } 10 \text{ Ohm} = 1.2 + 10 = 11.2 \text{ } \Omega$

37
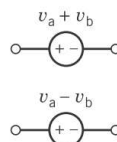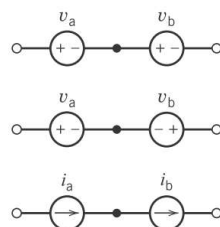
## Parallel and Series Voltage and Current Sources




Not allowed

Voltage source สามารถ  
ต่ออนุกรมกันได้

Current source จะต่ออนุกรม  
 กันไม่ได้ ถ้ากระแสไม่เท่ากัน  
 เพราะกระแสใน 1 Branch  
 จะมีค่าได้ 1 ค่าเท่านั้น

38
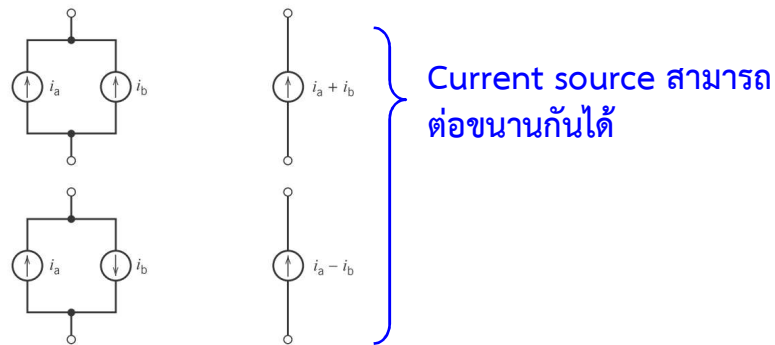
### Parallel and Series Voltage and Current Sources




Current source สามารถ  
ต่อขนานกันได้

Voltage source ที่มีค่าต่างกัน  
จะนำมาต่อขนานกันไม่ได้ เพราะ  
แรงดันตกคร่อม 1 Branch  
จะมีได้ 1 ค่าเท่านั้น

39

## 2.6 Voltmeters and Ammeters

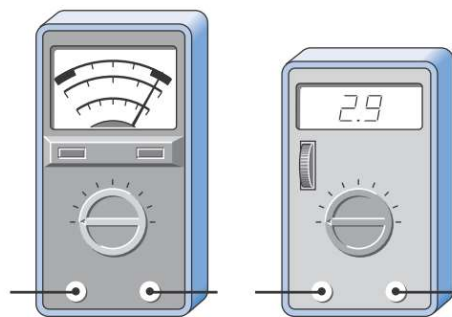


(a)

Analog Meter


(b)

Digital Meter


## 2.7 Multimeters

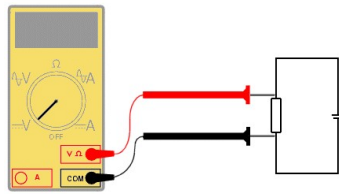

Using a multimeter  
to measure voltage

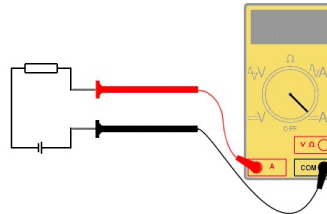

Using a multimeter  
to measure current

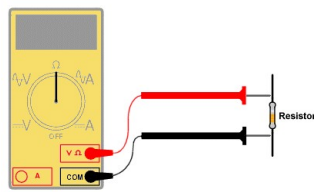


Using a multimeter  
to measure resistance



สายไฟฟ้า สีแดงคือ +  
สีอ่อนคือ +


สีดำคือ -  
สีเข้มคือ -

## 2.6 Voltmeters and Ammeters

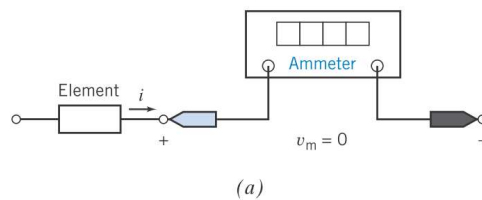

Ideal Ammeter


การต่อ Ammeter  
ต้องต่ออนุกรมกับ Load

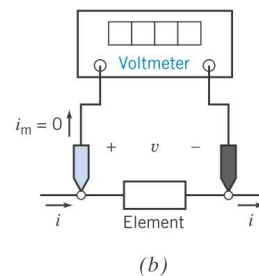

Ideal Voltmeter

การต่อ Voltmeter  
ต้องต่อขนานกับ Load


## 2.6 Voltmeters and Ammeters

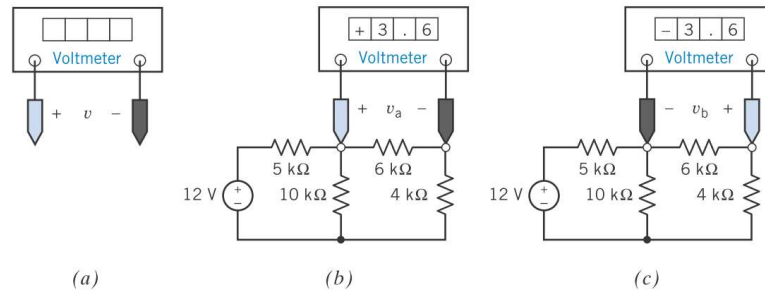

Using a voltmeter to measure voltage

การต่อ Voltmeter เราจะต่อขั้วบวกของ meter กับขั้วบวกของแหล่งจ่ายไฟฟ้า และต่อขั้วลบของ meter เข้ากับขั้วลบของแหล่งจ่าย  
 ถ้าแรงดันที่วัดได้เป็นบวก แสดงว่าแรงดันมีขั้วตามที่กำหนดไว้  
 ถ้าแรงดันที่วัดได้เป็นลบ แสดงว่าแรงดันมีขั้วตรงข้ามกับที่กำหนดไว้


## 2.6 Voltmeters and Ammeters

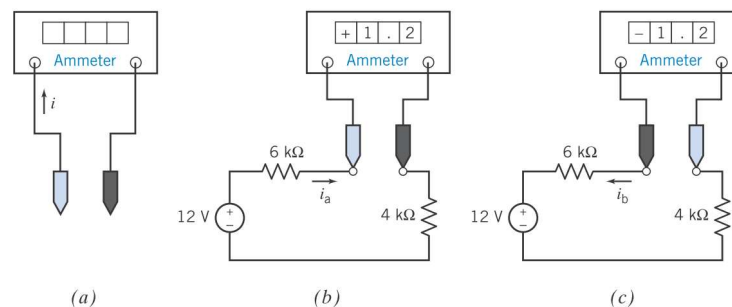


Using an ammeter to measure current

การต่อ Ammeter เราจะกำหนดให้กระแสไหลเข้าที่ขั้วบวกของ Ammeter และไหลออกที่ขั้วลบของ Ammeter  
 ถ้ากระแสที่วัดได้เป็นบวก แสดงว่ากระแสไหลตามทิศที่กำหนดไว้  
 ถ้ากระแสที่วัดได้เป็นลบ แสดงว่ากระแสไหลตรงข้ามกับทิศที่กำหนดไว้


## 2.8 Y- $\Delta$ Transformation

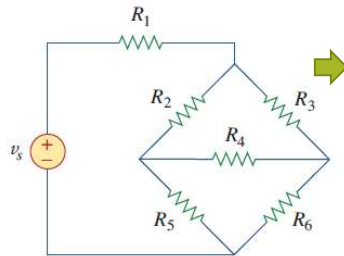

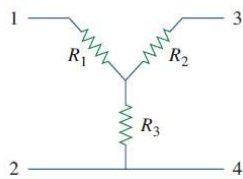ไม่ใช่ทั้งการต่อแบบอนุกรมและขนาน  
ต้องใช้การแปลง Y- $\Delta$  มาช่วย




การต่อแบบ Y

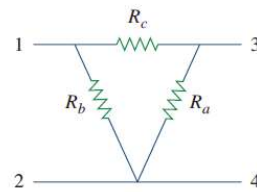


การต่อแบบ  $\Delta$

45

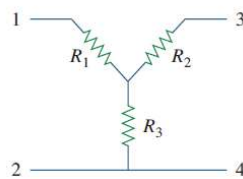

การต่อแบบ Y

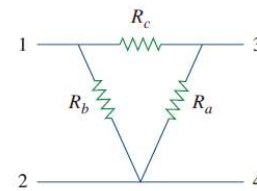

การต่อแบบ  $\Delta$

$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$

$$R_2 = \frac{R_c R_a}{R_a + R_b + R_c}$$

$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$


$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

46
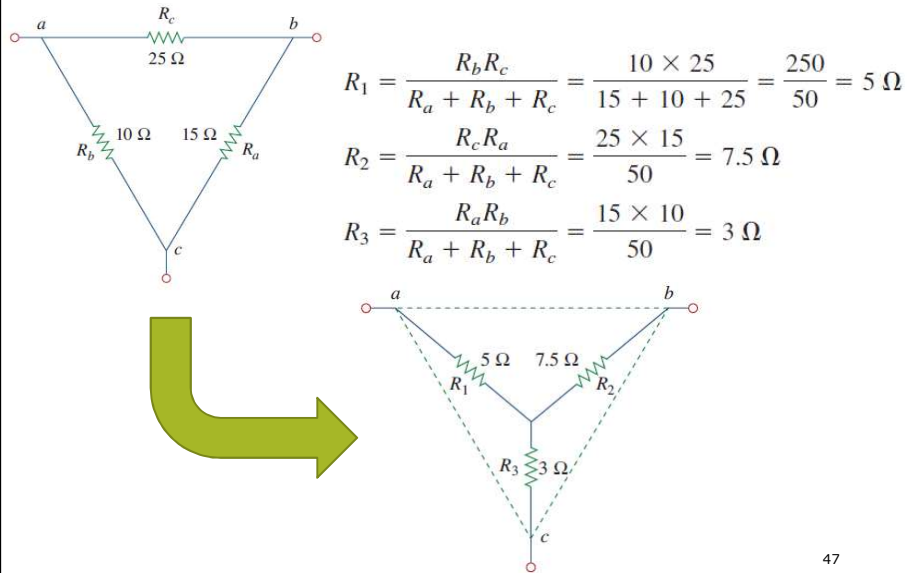
### Example 2.14


Convert the  $\Delta$  network in Fig. 2.50(a) to an equivalent Y network.



47

### Example 2.15

Obtain the equivalent resistance  $R_{ab}$  for the circuit in Fig. 2.52 and use it to find current  $i$ .

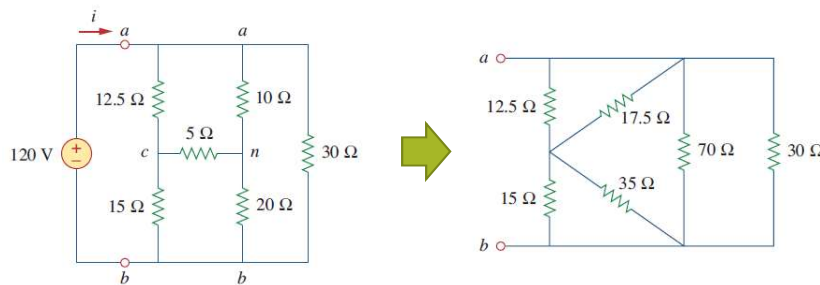

**Figure 2.52**  
For Example 2.15.

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1} = \frac{10 \times 20 + 20 \times 5 + 5 \times 10}{10}$$

$$= \frac{350}{10} = 35 \Omega$$


$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2} = \frac{350}{20} = 17.5 \Omega$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3} = \frac{350}{5} = 70 \Omega$$

48




### Example 2.15

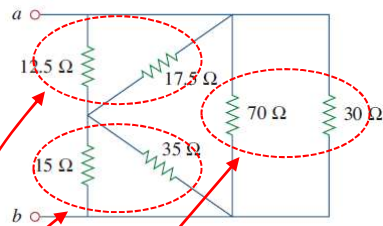

$$70 \parallel 30 = \frac{70 \times 30}{70 + 30} = 21 \Omega$$

$$12.5 \parallel 17.5 = \frac{12.5 \times 17.5}{12.5 + 17.5} = 7.292 \Omega$$
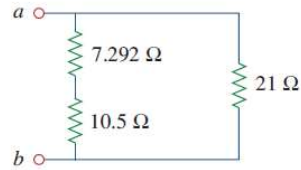
$$15 \parallel 35 = \frac{15 \times 35}{15 + 35} = 10.5 \Omega$$



$$\begin{aligned} R_{ab} &= (7.292 + 10.5) \parallel 21 \\ &= \frac{17.792 \times 21}{17.792 + 21} \\ &= 9.632 \Omega \end{aligned}$$

$$I = \frac{v_s}{R_{ab}} = \frac{120}{9.632} = 12.458 A$$

49