

# EN811100 LINEAR CIRCUIT ANALYSIS

---

## Chapter 10

### Sinusoidal Steady-State Analysis

Mar 10, 2563

C. K. Alexander – M. N. O. Sadiku  
Fundamentals of Electric Circuits, 5<sup>th</sup> Edition, The McGraw-Hill Companies 2013  
J. A. Svoboda – R. C. Dorf  
Introduction to Electric Circuits, 9<sup>th</sup> edition, John Wiley & Sons, Inc. 2014

1

## Sinusoidal Steady-State Analysis- Chapter 10


- 10.1 Basic Approach
- 10.2 Nodal Analysis
- 10.3 Mesh Analysis
- 10.4 Superposition Theorem
- 10.5 Source Transformation
- 10.6 Thevenin and Norton Equivalent Circuits

2

## 10.1 Basic Approach

### Steps to Analyze AC Circuits:

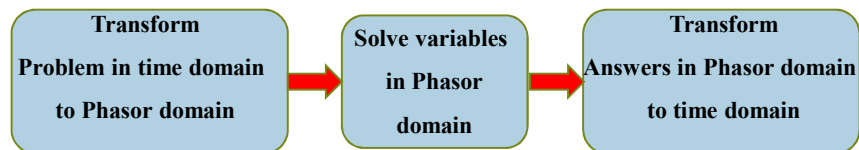
1. **Transform** the circuit to the **phasor or frequency domain**.
2. **Solve** the problem using circuit techniques (nodal analysis, mesh analysis, superposition, etc.).
3. **Transform** the resulting phasor to the time domain.



3

## 10.2 Nodal Analysis

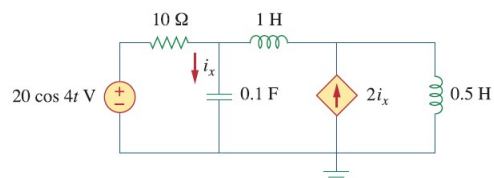**Example 10.1** Find  $i_x$  in the circuit of Fig. 10.1 using nodal analysis.




**วิธีทำ 1. แปลงเป็น Phasor**


$$20 \cos 4t \Rightarrow 20 \angle 0^\circ, \quad \omega = 4 \text{ rad/s}$$

$$1 \text{ H} \Rightarrow j\omega L = j4$$

$$0.5 \text{ H} \Rightarrow j\omega L = j2$$
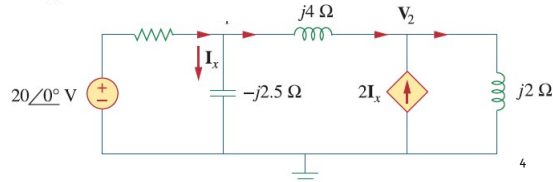
$$0.1 \text{ F} \Rightarrow \frac{1}{j\omega C} = -j2.5$$



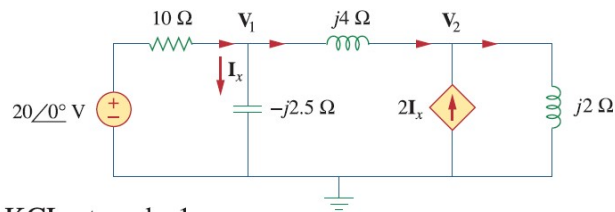

Applying KCL at node 1,

$$\frac{20 - V_1}{10} = \frac{V_1}{-j2.5} + \frac{V_1 - V_2}{j4} \Rightarrow (1 + j1.5)V_1 + j2.5V_2 = 20$$

At node 2,

$$2I_x + \frac{V_1 - V_2}{j4} = \frac{V_2}{j2} \quad \text{โดย} \quad I_x = \frac{V_1}{-j2.5}$$

จะได้

$$\frac{2V_1}{-j2.5} + \frac{V_1 - V_2}{j4} = \frac{V_2}{j2} \Rightarrow 11V_1 + 15V_2 = 0$$

5

$$(1 + j1.5)V_1 + j2.5V_2 = 20$$

$$11V_1 + 15V_2 = 0$$


จัดรูป Matrix

$$\begin{bmatrix} 1 + j1.5 & j2.5 \\ 11 & 15 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 20 \\ 0 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 1 + j1.5 & j2.5 \\ 11 & 15 \end{vmatrix} = 15 - j5$$

$$\Delta_1 = \begin{vmatrix} 20 & j2.5 \\ 0 & 15 \end{vmatrix} = 300 \Rightarrow V_1 = \frac{\Delta_1}{\Delta} = \frac{300}{15 - j5} = 18.97 \angle 18.43^\circ \text{ V}$$
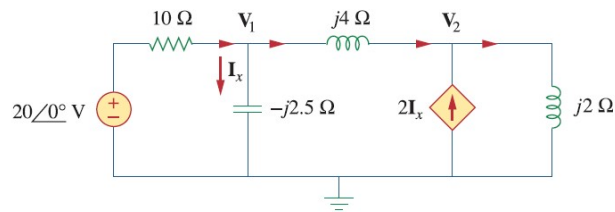
$$\Delta_2 = \begin{vmatrix} 1 + j1.5 & 20 \\ 11 & 0 \end{vmatrix} = -220 \Rightarrow V_2 = \frac{\Delta_2}{\Delta} = \frac{-220}{15 - j5} = 13.91 \angle 198.3^\circ \text{ V}$$



$$\mathbf{I}_x = \frac{\mathbf{V}_1}{-j2.5} = \frac{18.97 \angle 18.43^\circ}{2.5 \angle -90^\circ} = 7.59 \angle 108.4^\circ \text{ A}$$

Transforming this to the time domain,

$$i_x = 7.59 \cos(4t + 108.4^\circ) \text{ A}$$

7


**Example 10.2** Compute  $\mathbf{V}_1$  and  $\mathbf{V}_2$  in the circuit of Fig. 10.4.

วิธีทำ

ใช้ Supernode

$$3 = \frac{\mathbf{V}_1}{-j3} + \frac{\mathbf{V}_2}{j6} + \frac{\mathbf{V}_2}{12}$$
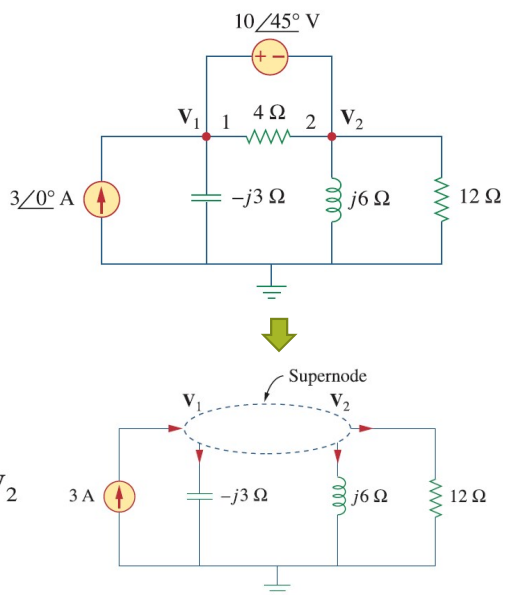
$$36 = j4\mathbf{V}_1 + (1 - j2)\mathbf{V}_2$$



$V_1 = V_2 + 10\angle 45^\circ$

แทนลงไป

$36 = j4V_1 + (1 - j2)V_2$

$36 - 40\angle 135^\circ = (1 + j2)V_2$

จะได้

$V_2 = 31.41\angle -87.18^\circ \text{ V}$

$V_1 = V_2 + 10\angle 45^\circ = 25.78\angle -70.48^\circ \text{ V}$

9

### Example 10.3 10.3 Mesh Analysis

Determine current  $I_o$  in the circuit of Fig. 10.7 using mesh analysis.

วิธีทำ

KVL Mesh 1

$(8 + j10 - j2)I_1 - (-j2)I_2 - j10I_3 = 0$

KVL Mesh 2

$(4 - j2 - j2)I_2 - (-j2)I_1 - (-j2)I_3 + 20\angle 90^\circ = 0$

จะได้

$(8 + j8)I_1 + j2I_2 = j50$

$j2I_1 + (4 - j4)I_2 = -j20 - j10$

$I_3 = 5\angle 0^\circ$

10

$$(8 + j8)\mathbf{I}_1 + j2\mathbf{I}_2 = j50$$

$$j2\mathbf{I}_1 + (4 - j4)\mathbf{I}_2 = -j20 - j10$$

จัดรูป Matrix

$$\begin{bmatrix} 8 + j8 & j2 \\ j2 & 4 - j4 \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix} = \begin{bmatrix} j50 \\ -j30 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 8 + j8 & j2 \\ j2 & 4 - j4 \end{vmatrix} = 32(1 + j)(1 - j) + 4 = 68$$

$$\Delta_2 = \begin{vmatrix} 8 + j8 & j50 \\ j2 & -j30 \end{vmatrix} = 340 - j240 = 416.17 \angle -35.22^\circ$$

จะได้

$$\mathbf{I}_2 = \frac{\Delta_2}{\Delta} = \frac{416.17 \angle -35.22^\circ}{68} = 6.12 \angle -35.22^\circ \text{ A}$$


$$\mathbf{I}_o = -\mathbf{I}_2 = 6.12 \angle 144.78^\circ \text{ A}$$

11

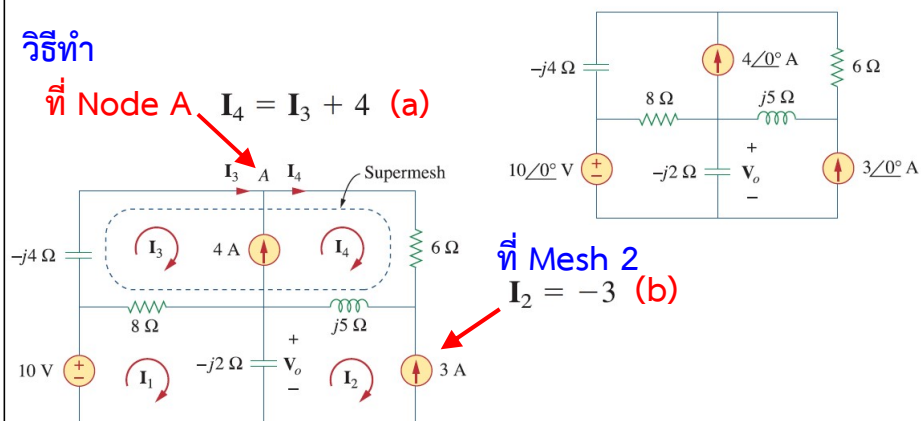**Example 10.4** Solve for  $\mathbf{V}_o$  in the circuit of Fig. 10.9 using mesh analysis.

วิธีทำ

ที่ Node A  $\mathbf{I}_4 = \mathbf{I}_3 + 4$  (a)



ที่ Mesh 2  
 $\mathbf{I}_2 = -3$  (b)

KVL Mesh 1  $-10 + (8 - j2)\mathbf{I}_1 - (-j2)\mathbf{I}_2 - 8\mathbf{I}_3 = 0$

$$(8 - j2)\mathbf{I}_1 + j2\mathbf{I}_2 - 8\mathbf{I}_3 = 10 \quad \text{(c)}$$

KVL Supermesh

$$(8 - j4)\mathbf{I}_3 - 8\mathbf{I}_1 + (6 + j5)\mathbf{I}_4 - j5\mathbf{I}_2 = 0 \quad \text{(d)}$$

$$\mathbf{I}_2 = -3$$

$$(c) (8 - j2)\mathbf{I}_1 + j2\mathbf{I}_2 - 8\mathbf{I}_3 = 10 \Rightarrow (8 - j2)\mathbf{I}_1 - 8\mathbf{I}_3 = 10 + j6 \quad (e)$$

$$\mathbf{I}_4 = \mathbf{I}_3 + 4$$

$$\mathbf{I}_2 = -3$$

$$(d) (8 - j4)\mathbf{I}_3 - 8\mathbf{I}_1 + (6 + j5)\mathbf{I}_4 - j5\mathbf{I}_2 = 0$$

$$-8\mathbf{I}_1 + (14 + j)\mathbf{I}_3 = -24 - j35 \quad (f)$$

จัดสมการ (e), (f) ในรูป Matrix

$$\begin{bmatrix} 8 - j2 & -8 \\ -8 & 14 + j \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_3 \end{bmatrix} = \begin{bmatrix} 10 + j6 \\ -24 - j35 \end{bmatrix}$$

13

$$\begin{bmatrix} 8 - j2 & -8 \\ -8 & 14 + j \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_3 \end{bmatrix} = \begin{bmatrix} 10 + j6 \\ -24 - j35 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 8 - j2 & -8 \\ -8 & 14 + j \end{vmatrix} = 112 + j8 - j28 + 2 - 64 = 50 - j20$$

$$\Delta_1 = \begin{vmatrix} 10 + j6 & -8 \\ -24 - j35 & 14 + j \end{vmatrix} = 140 + j10 + j84 - 6 - 192 - j280 = -58 - j186$$

จะได้

$$\mathbf{I}_1 = \frac{\Delta_1}{\Delta} = \frac{-58 - j186}{50 - j20} = 3.618 \angle 274.5^\circ \text{ A}$$

$$\begin{aligned} \mathbf{V}_o &= -j2(\mathbf{I}_1 - \mathbf{I}_2) = -j2(3.618 \angle 274.5^\circ + 3) \\ &= -7.2134 - j6.568 = 9.756 \angle 222.32^\circ \text{ V} \end{aligned}$$

14

วิธีใช้คอมพิวเตอร์ช่วยคำนวณ

นำสมการ (c), (b), (d), (a) มาเขียนเป็น Matrix form

$$\begin{bmatrix} 8-j2 & j2 & -8 & 0 \\ 0 & 1 & 0 & 0 \\ -8 & -j5 & 8-j4 & 6+j5 \\ 0 & 0 & -1 & 1 \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \\ \mathbf{I}_3 \\ \mathbf{I}_4 \end{bmatrix} = \begin{bmatrix} 10 \\ -3 \\ 0 \\ 4 \end{bmatrix} \Rightarrow \mathbf{AI} = \mathbf{B}$$

จะได้  $\mathbf{I} = \mathbf{A}^{-1}\mathbf{B}$

MATLAB Code

```
>> A = [(8-j*2) j*2 -8 0;
        0 1 0 0;
        -8 -j*5 (8-j*4) (6+j*5);
        0 0 -1 1];
>> B = [10 -3 0 4]';
>> I = inv(A)*B
```

15

MATLAB Code

```
>> A = [(8-j*2) j*2 -8 0;
        0 1 0 0;
        -8 -j*5 (8-j*4) (6+j*5);
        0 0 -1 1];
>> B = [10 -3 0 4]';
>> I = inv(A)*B
I =
    0.2828 - 3.6069i
   -3.0000
   -1.8690 - 4.4276i
    2.1310 - 4.4276i
>> Vo = -2*j*(I(1) - I(2))
Vo =
   -7.2138 - 6.5655i
```

16



## 10.4 Superposition Theorem

When a circuit has sources operating at different frequencies,

- The separate phasor circuit for each frequency must be solved independently, and
- The total response is the sum of time-domain responses of all the individual phasor circuits.

17

### Example 10.5

Use the superposition theorem to find  $\mathbf{I}_o$  in the circuit in Fig. 10.7.

วิธีทำ


วงจรนี้มี Source 2 ตัวคือ

$5\angle 0^\circ \text{ A}$  และ  $20\angle 90^\circ \text{ V}$

1. ให้ Voltage source ON

และ Current source OFF (Open circuit) และหากระแส  $\mathbf{I}'_o$

อันเนื่องมาจาก Voltage source ทำงาน

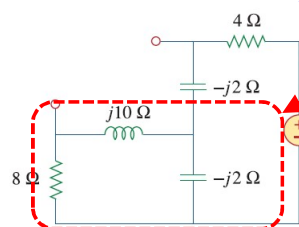

$$\mathbf{Z} = \frac{-j2(8 + j10)}{-2j + 8 + j10} = 0.25 - j2.25$$

$$\mathbf{I}'_o = \frac{j20}{4 - j2 + \mathbf{Z}} = \frac{j20}{4.25 - j4.25}$$

$$\mathbf{I}'_o = -2.353 + j2.353$$

18

2. ให้ Voltage source OFF (Short circuit) และ Current source ON และหากระแส  $I''_0$  อันเนื่องมาจาก Current source ทำงาน


KVL Mesh 1

$$(8 + j8)I_1 - j10I_3 + j2I_2 = 0 \quad (a)$$

KVL Mesh 2

$$(4 - j4)I_2 + j2I_1 + j2I_3 = 0 \quad (b)$$

Current Mesh 3 =  $I_3 = 5$

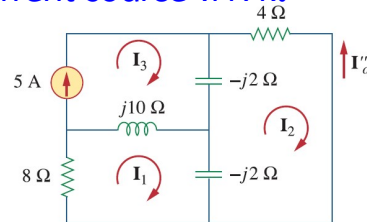

$$(4 - j4)I_2 + j2I_1 + j10 = 0$$

$$I_1 = (2 + j2)I_2 - 5$$

$$(8 + j8)I_1 - j10I_3 + j2I_2 = 0 \quad (a)$$

$$(8 + j8)[(2 + j2)I_2 - 5] - j50 + j2I_2 = 0$$

จะได้ 
$$I_2 = \frac{90 - j40}{34} = 2.647 - j1.176$$

19

จะได้ 
$$I''_o = -I_2 = -2.647 + j1.176$$

กระแส  $I_0$  โดยรวมคือกระแส  $I'_0$  อันเนื่องมาจาก Voltage source บวกกับกระแส  $I''_0$  อันเนื่องมาจาก Current source

จะได้


$$I_o = I'_o + I''_o = -5 + j3.529 = 6.12 \angle 144.78^\circ \text{ A}$$

คำตอบนี้ตรงกับคำตอบในตัวอย่างที่ 10.3

20
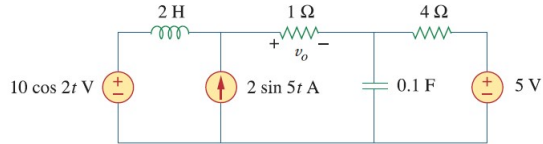
### Example 10.6

Find  $v_o$  of the circuit of Fig. 10.13 using the superposition theorem.



วิธีทำ


วงจรนี้มี Source 3 ตัว แต่ละตัวมีความถี่ไม่เท่ากัน

$$10 \cos 2t \rightarrow \omega = 2$$

$$5 \sin 5t \rightarrow \omega = 5$$

$$5 \text{ V} \rightarrow \omega = 0$$

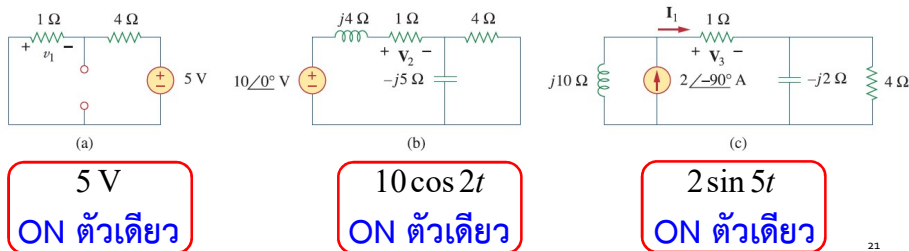เวลาคำนวณจึงต้องแยกกันคำนวณโดยใช้หลักการ Superposition




1. ให้ Voltage source 5 V ON, Current source ที่เหลือให้เป็น Open circuit, Voltage source ที่เหลือเป็น Short Circuit  
ในกรณีนี้เป็น DC Source,  $\omega=0$ ,


$$z_L = j\omega L = 0$$

$$z_C = \frac{1}{j\omega C} = \infty$$

จะได้วงจรเป็น

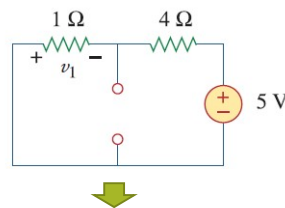

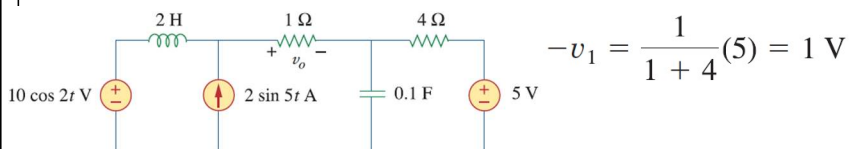ใช้ Voltage Divider หาแรงดัน  
ตกคร่อม R 1 ohm



2. ให้ Voltage source  $10\cos(2t)$  ON, Current source ที่เหลือให้เป็น Open circuit, Voltage source ที่เหลือเป็น Short Circuit ในกรณีนี้  $\omega=2$ ,

$$z_L = j\omega L = j2 \times 2 = j4 \Omega$$


$$z_C = \frac{1}{j\omega C} = \frac{1}{j2 \times 0.1} = -j5 \Omega$$

$$Z = -j5 \parallel 4 = \frac{-j5 \times 4}{4 - j5} = 2.439 - j1.951$$

ใช้ Voltage Divider หาแรงดันตกคร่อม R 1  $\Omega$

$$V_2 = \frac{1}{1 + j4 + Z} (10 \angle 0^\circ) = \frac{10}{3.439 + j2.049} = 2.498 \angle -30.79^\circ$$

$$v_2 = 2.498 \cos(2t - 30.79^\circ)$$

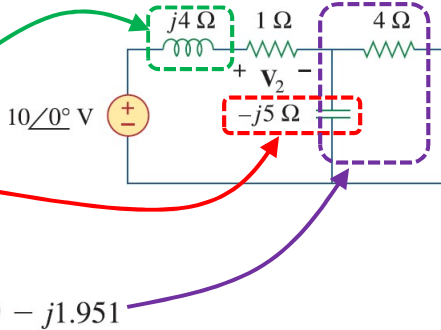

23

3. ให้ Current source  $2\sin(5t)$  ON, Current source ที่เหลือให้เป็น Open circuit, Voltage source ที่เหลือเป็น Short Circuit ในกรณีนี้  $\omega=5$ ,

$$z_L = j\omega L = j5 \times 2$$

$$= j10 \Omega$$

$$z_C = \frac{1}{j\omega C} = \frac{1}{j5 \times 0.1} = -j2 \Omega$$


$$Z_1 = -j2 \parallel 4 = \frac{-j2 \times 4}{4 - j2} = 0.8 - j1.6 \Omega$$

ใช้ Current Divider  
หากระแสที่ผ่าน R 1  $\Omega$


$$\Rightarrow I_1 = \frac{j10}{j10 + 1 + Z_1} (2 \angle -90^\circ) \text{ A}$$

$$V_3 = I_1 \times 1 = \frac{j10}{1.8 + j8.4} (-j2) = 2.328 \angle -80^\circ \text{ V}$$
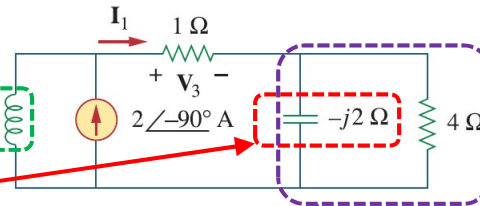
$$v_3 = 2.33 \cos(5t - 80^\circ) = 2.33 \sin(5t + 10^\circ) \text{ V}$$



24

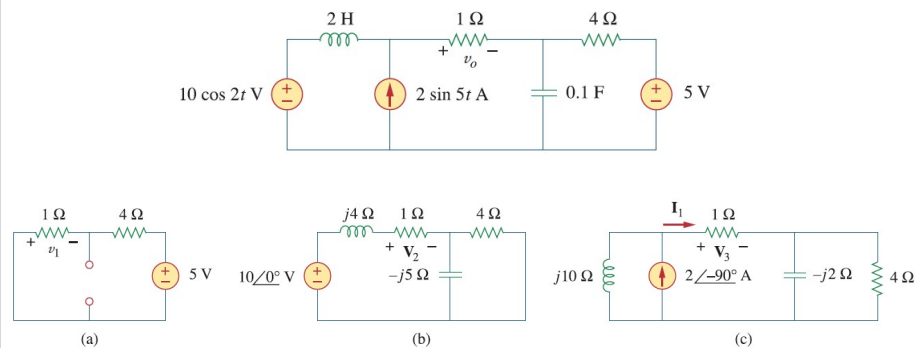

ใช้หลักการ Superposition


$$v_o = v_1 + v_2 + v_3$$

$$v_o(t) = -1 + 2.498 \cos(2t - 30.79^\circ) + 2.33 \sin(5t + 10^\circ) \text{ V}$$

25
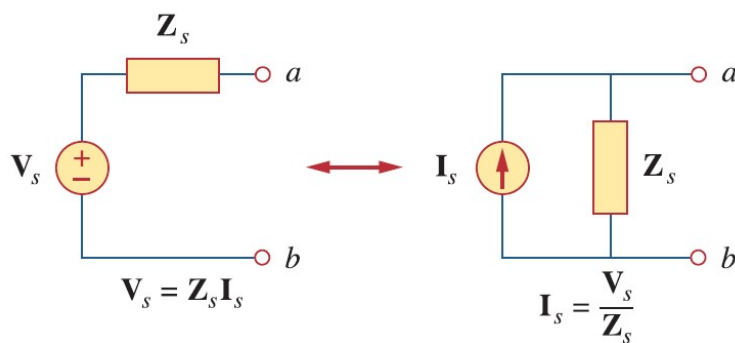
## 10.5 Source Transformation

เราสามารถแปลง Voltage source เป็น Current source หรือ  
แปลงจาก Current source เป็น Voltage source โดยใช้สูตรดังนี้



26

### Example 10.7


Calculate  $V_x$  in the circuit of Fig. 10.17 using the method of source transformation.

วิธีทำ

แปลง Voltage source  
เป็น Current source

$$I_s = \frac{20 \angle -90^\circ}{5} = 4 \angle -90^\circ = -j4 \text{ A}$$
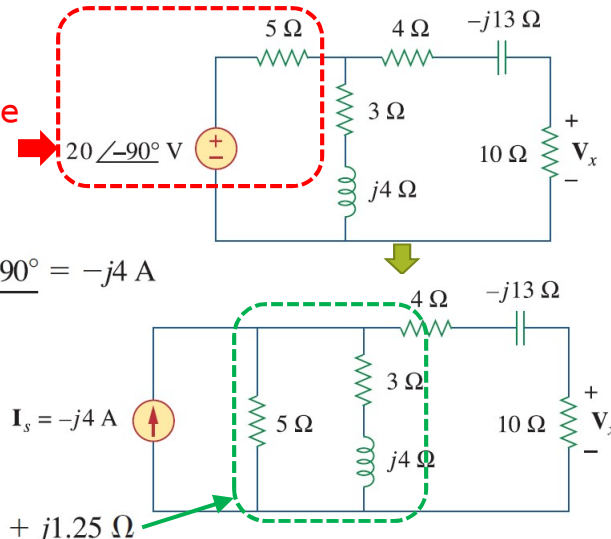
$$Z_1 = \frac{5(3 + j4)}{8 + j4} = 2.5 + j1.25 \Omega$$




$$Z_1 = \frac{5(3 + j4)}{8 + j4} = 2.5 + j1.25 \Omega$$

แปลง Current source  
กลับเป็น Voltage source


$$V_s = I_s Z_1 = -j4(2.5 + j1.25) = 5 - j10 \text{ V}$$

ใช้ Voltage Divider
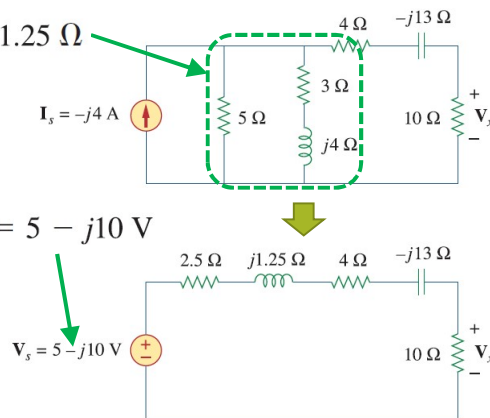
$$V_x = \frac{10}{10 + 2.5 + j1.25 + 4 - j13} (5 - j10) = 5.519 \angle -28^\circ \text{ V}$$


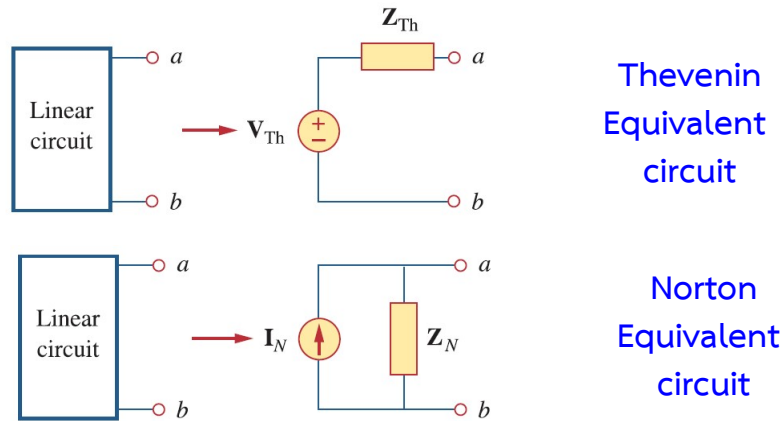
## 10.6 Thevenin and Norton Equivalent Circuits




$$V_{Th} = Z_N I_N, \quad Z_{Th} = Z_N$$

29
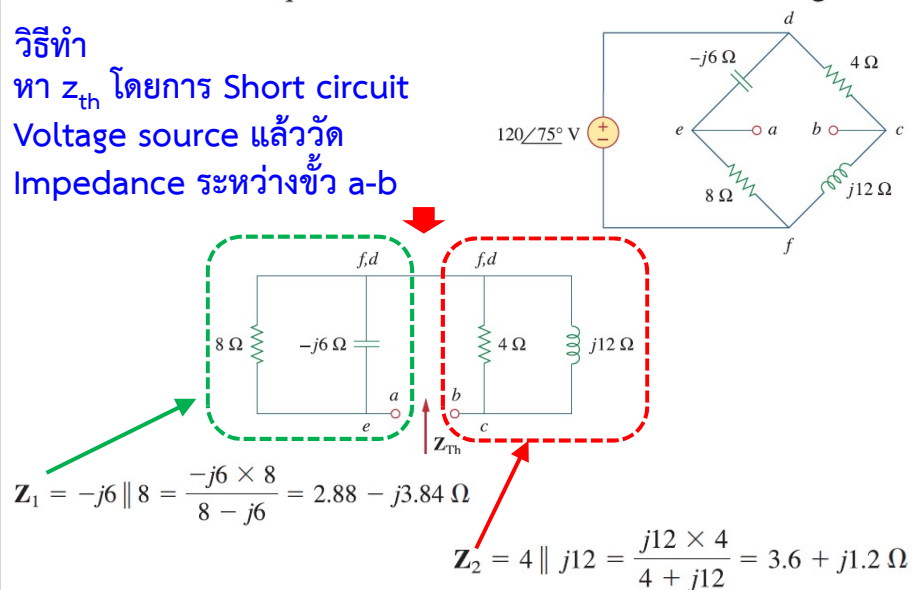
### Example 10.8

Obtain the Thevenin equivalent at terminals  $a-b$  of the circuit in Fig. 10.22.

วิธีทำ  
หา  $z_{th}$  โดยการ Short circuit  
Voltage source แล้ววัด  
Impedance ระหว่างขั้ว  $a-b$



$Z_1$  and  $Z_2$  are in parallel.  $Z_{Th} = Z_1 + Z_2 = 6.48 - j2.64 \Omega$

หาคะแส  $I_1$  และ  $I_2$

$$I_1 = \frac{120 \angle 75^\circ}{8 - j6} \text{ A},$$

$$I_2 = \frac{120 \angle 75^\circ}{4 + j12} \text{ A}$$

ใช้ KVL ใน Loop bcdeab

$$V_{Th} - 4I_2 + (-j6)I_1 = 0$$

จะได้  $v_{th}$  ระหว่างขั้ว a-b

$$V_{Th} = 4I_2 + j6I_1 = \frac{480 \angle 75^\circ}{4 + j12} + \frac{720 \angle 75^\circ + 90^\circ}{8 - j6}$$

หาคะแส  $I_1$  และ  $I_2$

$$I_1 = \frac{120 \angle 75^\circ}{8 - j6} \text{ A},$$

$$I_2 = \frac{120 \angle 75^\circ}{4 + j12} \text{ A}$$

จะได้  $v_{th}$  ระหว่างขั้ว a-b

$$V_{Th} = 4I_2 + j6I_1 = \frac{480 \angle 75^\circ}{4 + j12} + \frac{720 \angle 75^\circ + 90^\circ}{8 - j6}$$



$$= 37.95 \angle 3.43^\circ + 72 \angle 201.87^\circ$$

$$= -28.936 - j24.55 = 37.95 \angle 220.31^\circ \text{ V}$$


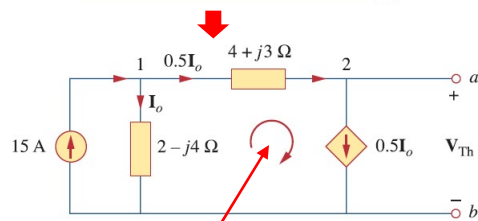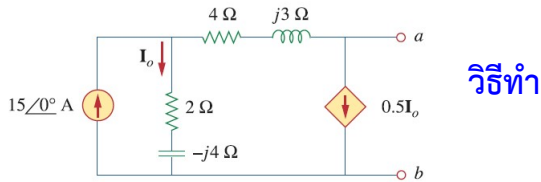
### Example 10.9

Find the Thevenin equivalent of the circuit in Fig. 10.25 as seen from terminals  $a-b$ .



KCL ที่ Node 1

$$15 = I_o + 0.5I_o$$


$$I_o = 10 \text{ A}$$

ใช้ KVL ใน Loop นี้  $-I_o(2 - j4) + 0.5I_o(4 + j3) + V_{Th} = 0$

จะได้  $V_{Th} = 10(2 - j4) - 5(4 + j3) = -j55$

33

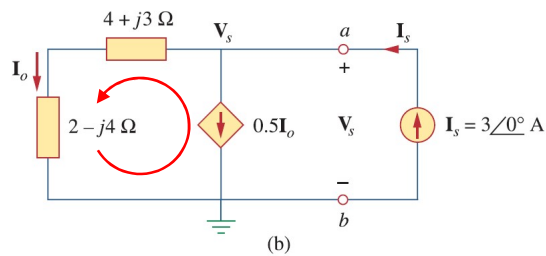หาค่า  $z_{th}$  โดยเอา Independent source ออกไป แล้วนำ Current Source  $I = 3\angle 0^\circ \text{ A}$  มาต่อที่ขั้ว  $a-b$  แล้ววัดแรงดันที่ขั้ว  $a-b$



KCL ที่ Node a  $3 = I_o + 0.5I_o \Rightarrow I_o = 2 \text{ A}$


KCL ที่ Loop 1  $V_s = I_o(4 + j3 + 2 - j4) = 2(6 - j)$

$$Z_{Th} = \frac{V_s}{I_s} = \frac{2(6 - j)}{3} = 4 - j0.6667 \Omega$$

34

### Practice Problem 10.1

Using nodal analysis, find  $v_1$  and  $v_2$  in the circuit of Fig. 10.3.

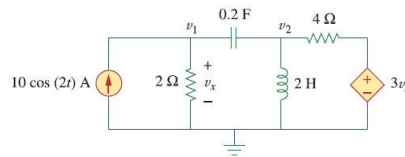


**Figure 10.3**

For Practice Prob. 10.1.

**Answer:**  $v_1(t) = 11.325 \cos(2t + 60.01^\circ) \text{ V}$ ,  
 $v_2(t) = 33.02 \cos(2t + 57.12^\circ) \text{ V}$ .

Calculate  $V_1$  and  $V_2$  in the circuit shown in Fig. 10.6.

### Practice Problem 10.2

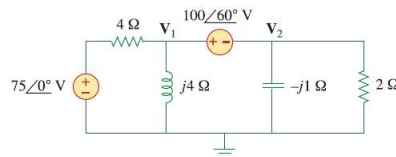

**Figure 10.6**


For Practice Prob. 10.2.

**Answer:**  $V_1 = 96.8 \angle 69.66^\circ \text{ V}$ ,  $V_2 = 16.88 \angle 165.72^\circ \text{ V}$ .

### Practice Problem 10.3

Find  $I_o$  in Fig. 10.8 using mesh analysis.

**Answer:**  $5.969 \angle 65.45^\circ \text{ A}$ .

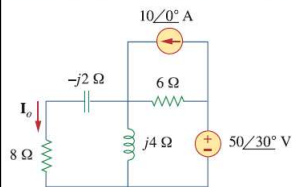


**Figure 10.8**

For Practice Prob. 10.3.

Calculate current  $I_o$  in the circuit of Fig. 10.11.
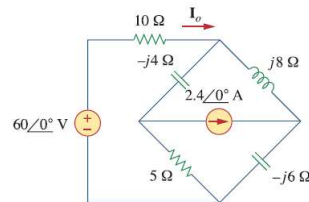
### Practice Problem 10.4

**Answer:**  $6.089 \angle 5.94^\circ \text{ A}$ .




**Practice Problem 10.5**

Find current  $\mathbf{I}_o$  in the circuit of Fig. 10.8 using the superposition theorem.

**Answer:**  $5.97/65.45^\circ$  A.

**Practice Problem 10.6**

Calculate  $v_o$  in the circuit of Fig. 10.15 using the superposition theorem.

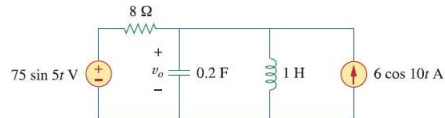

**Figure 10.15**


For Practice Prob. 10.6.

**Answer:**  $11.577 \sin(5t - 81.12^\circ) + 3.154 \cos(10t - 86.24^\circ)$  V.

37

**Practice Problem 10.7**

Find  $\mathbf{I}_o$  in the circuit of Fig. 10.19 using the concept of source transformation.

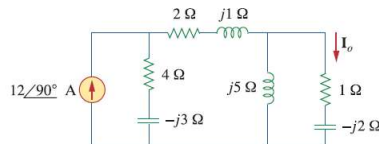


**Figure 10.19**

For Practice Prob. 10.7.

**Answer:**  $9.863/99.46^\circ$  A.

**Practice Problem 10.8**

Find the Thevenin equivalent at terminals  $a$ - $b$  of the circuit in Fig. 10.24.

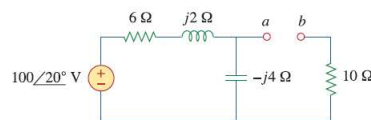

**Figure 10.24**

For Practice Prob. 10.8.


**Answer:**  $\mathbf{Z}_{Th} = 12.4 - j3.2 \Omega$ ,  $\mathbf{V}_{Th} = 63.24/-51.57^\circ$  V.

38

Determine the Thevenin equivalent of the circuit in Fig. 10.27 as seen from the terminals  $a$ - $b$ .

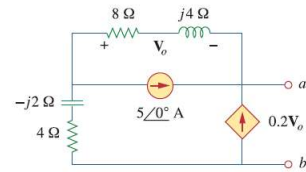
### Practice Problem 10.9

**Answer:**  $Z_{Th} = 4.473 \angle -7.64^\circ \Omega$ ,  $V_{Th} = 7.35 \angle 72.9^\circ \text{ V}$ .



### Practice Problem 10.10

Determine the Norton equivalent of the circuit in Fig. 10.30 as seen from terminals  $a$ - $b$ . Use the equivalent to find  $I_o$ .

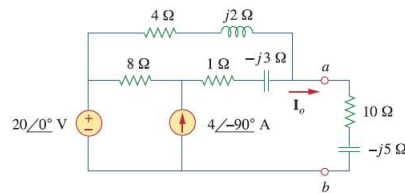

**Figure 10.30**

For Practice Prob. 10.10 and Prob. 10.35.

**Answer:**  $Z_N = 3.176 + j0.706 \Omega$ ,  $I_N = 8.396 \angle -32.68^\circ \text{ A}$ ,  $I_o = 1.9714 \angle -2.10^\circ \text{ A}$ .