

# EN811100 LINEAR CIRCUIT ANALYSIS

---

Chapter 1  
Basic Concepts  
Dec 20, 2019


C. K. Alexander – M. N. O. Sadiku  
Fundamentals of Electric Circuits, 5<sup>th</sup> Edition, The McGraw-Hill Companies 2013  
J. A. Svoboda – R. C. Dorf  
Introduction to Electric Circuits, 9<sup>th</sup> edition, John Wiley & Sons, Inc. 2014 <sub>1</sub>

## Basic Concepts - Chapter 1


- 1.1 Introduction.**
- 1.2 Systems of Units.**
- 1.3 Electric Charge.**
- 1.4 Current.**
- 1.5 Voltage.**
- 1.6 Power and Energy.**
- 1.7 Circuit Elements.**
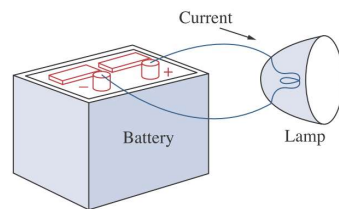
## 1.1 Introduction

An **electric circuit** is an interconnection of electrical elements.




A simple electric circuit.

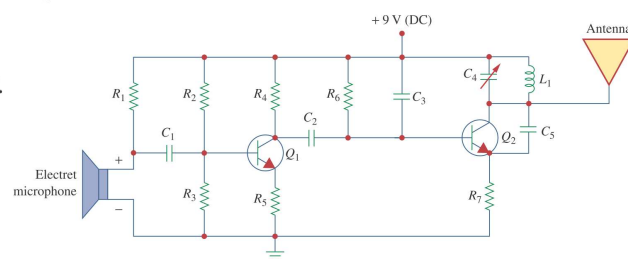


Electric circuit of a radio transmitter.

## 1.1 Introduction


### Power System

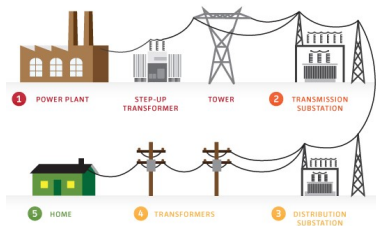


### Electronic System

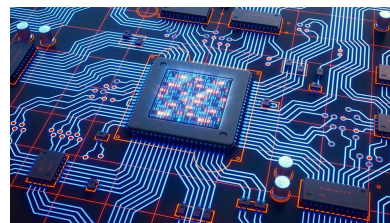


### Communication System

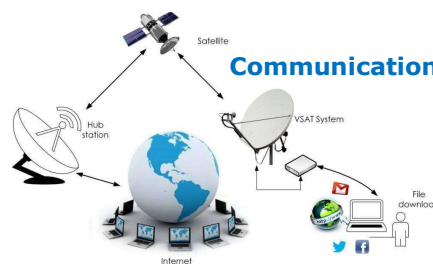

## 1.1 Introduction

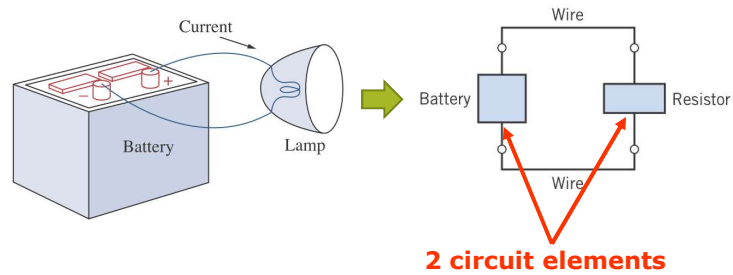

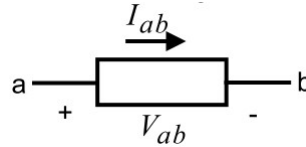**A general two-terminal electrical element**



5

## 1.2 System of Units

**SI** is *Système International d'Unités* or the International System of Units.

**Table 1.3-1 SI Base Units**

QUANTITY	SI UNIT	
	NAME	SYMBOL
Length	meter	m
Mass	kilogram	kg
Time	second	s
Electric current	ampere	A
Thermodynamic temperature	kelvin	K
Amount of substance	mole	mol
Luminous intensity	candela	cd

6

## 1.2 System of Units

**Table 1.3-2 Derived Units in SI**

QUANTITY	UNIT NAME	FORMULA	SYMBOL
Acceleration — linear	meter per second per second	$\text{m/s}^2$	
Velocity — linear	meter per second	$\text{m/s}$	
Frequency	hertz	$\text{s}^{-1}$	Hz
Force	newton	$\text{kg} \cdot \text{m/s}^2$	N
Pressure or stress	pascal	$\text{N/m}^2$	Pa
Density	kilogram per cubic meter	$\text{kg/m}^3$	
Energy or work	joule	$\text{N} \cdot \text{m}$	J
Power	watt	$\text{J/s}$	W
Electric charge	coulomb	$\text{A} \cdot \text{s}$	C
Electric potential	volt	$\text{W/A}$	V
Electric resistance	ohm	$\text{V/A}$	$\Omega$
Electric conductance	siemens	$\text{A/V}$	S
Electric capacitance	farad	$\text{C/V}$	F
Magnetic flux	weber	$\text{V} \cdot \text{s}$	Wb
Inductance	henry	$\text{Wb/A}$	H

7


## 1.2 System of Units

**Table 1.3-3 SI Prefixes**


MULTIPLE	PREFIX	SYMBOL
$10^{12}$	tera	T
$10^9$	giga	G
$10^6$	mega	M
$10^3$	kilo	k
$10^{-2}$	centi	c
$10^{-3}$	milli	m
$10^{-6}$	micro	$\mu$
$10^{-9}$	nano	n
$10^{-12}$	pico	p
$10^{-15}$	femto	f

8

## 1.3 Electric Charges

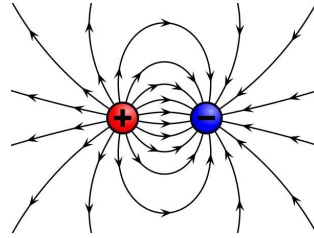

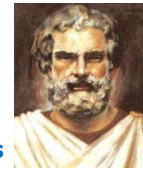- **Charge** is an electrical property of the atomic particles of which matter consists, measured in **coulombs (C)**.
- The charge **e** on one electron is negative and equal in magnitude to  $1.602 \times 10^{-19} \text{ C}$  which is called as **electronic charge**. The charges that occur in nature are **integral multiples** of the electronic charge.




**Thales of Miletus**  
(640 – 546 B.C.)

9
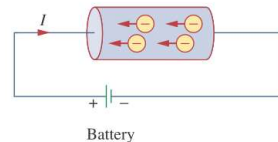
## 1.4 Current

ค่ากระแสไฟฟ้าคือปริมาณประจุที่เคลื่อนที่ผ่านแท่งตัวนำในระยะเวลา 1 วินาที



**Electric current** is the time rate of change of charge, measured in amperes (A).


- Electric current

$$i(t) = \frac{dq}{dt}$$

The unit of ampere can be derived as  $1 \text{ A} = 1 \text{ C/s}$ .




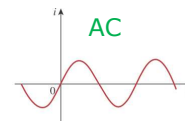- A **direct current (dc)** is a current that remains constant with time.
- An **alternating current (ac)** is a current that varies sinusoidally with time. (reverse direction)



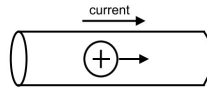
## 1.4 Current

The flow of current is conventionally represented as a flow of positive charges.



- The direction of current flow

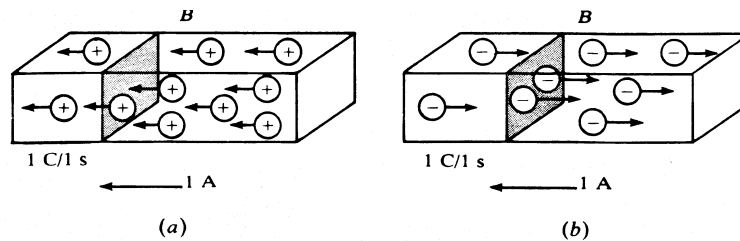


Positive ions

Negative ions

11

## 1.4 Current

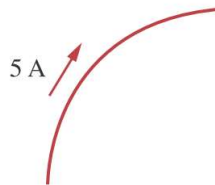

### Example 1

A conductor has a constant current of 5 A.

How many electrons pass a fixed point on the conductor in one minute?

12

## 1.4 Current

### Solution

Total no. of charges pass in 1 min is given by

$$5 \text{ A} = (5 \text{ C/s})(60 \text{ s/min}) = 300 \text{ C/min}$$

Total no. of electrons pass in 1 min is given

$$\frac{300 \text{ C/min}}{1.602 \times 10^{-19} \text{ C/electron}} = 1.87 \times 10^{21} \text{ electrons/min}$$

13

### Example 2 Charge from Current

Find the charge that has entered the terminal of an element from  $t = 0$  s to  $t = 3$  s when the current entering the element is as shown in Figure 1.2-6.

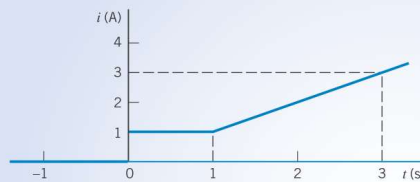


FIGURE 1.2-6 Current waveform for Example 1.2-2.

### **Solution**

From Figure 1.2-6, we can describe  $i(t)$  as

$$i(t) = \begin{cases} 0 & t < 0 \\ 1 & 0 \leq t \leq 1 \\ t & t > 1 \end{cases}$$

Using Eq. 1.2-2, we have

$$\begin{aligned} q &= \int_{-\infty}^t i \, d\tau = \int_0^t i \, d\tau + q(0) & q(3) - q(0) &= \int_0^3 i(t) \, dt = \int_0^1 1 \, dt + \int_1^3 t \, dt \\ & & &= \left. t \right|_0^1 + \left. \frac{t^2}{2} \right|_1^3 = 1 + \frac{1}{2}(9 - 1) = 5 \text{ C} \end{aligned}$$

Alternatively, we note that integration of  $i(t)$  from  $t = 0$  to  $t = 3$  s simply requires the calculation of the area under the curve shown in Figure 1.2-6. Then, we have

$$q = 1 + 2 \times 2 = 5 \text{ C}$$

14

## 1.5 Voltage

ค่าแรงดันไฟฟ้าคือพลังงานที่ต้องใช้ในการเคลื่อนที่ประจุ 1 หน่วย ผ่านจากขั้วต้นทางไปยังขั้วปลายทาง

- Voltage (or potential difference) is the **energy** required to move a **unit charge** through an element, measured in volts (V).
- Mathematically,

$W = \text{Work}$

$$v_{ab} = \frac{dw}{dq} \quad 1.2$$

- $w$  is energy in joules (J) and  $q$  is charge in coulomb (C).


- Electric voltage,  $v_{ab}$ , is always **across the circuit element** or **between two points in a circuit**.

- $v_{ab} > 0$  means the potential of **a** is higher than potential of **b**.
- $v_{ab} < 0$  means the potential of **a** is lower than potential of **b**.

15
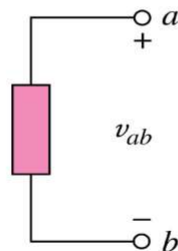
## 1.5 Voltage

- The plus (+) and minus (-) sign are used to define voltage polarity.
- The assumption is that the potential of the terminal with (+) polarity is higher than the potential of the terminal with (-) polarity by the amount of voltage drop.




- The polarity assignment is somewhat arbitrary! Is this a scientific statement?!! What do you mean by arbitrary?!!!

16


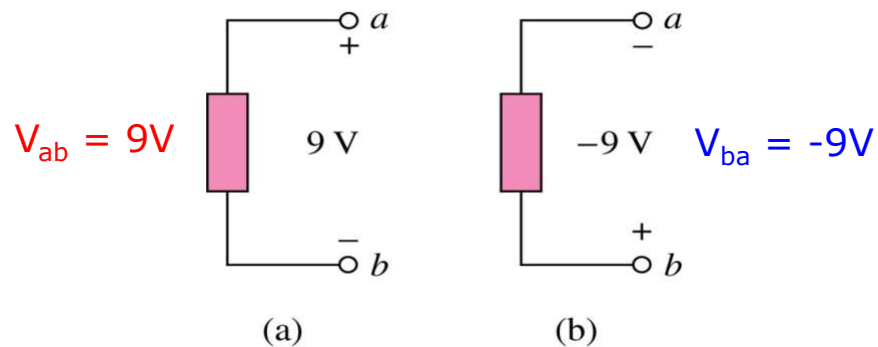
## 1.5 Voltage

- Figures (a) and (b) are two equivalent representation of the same voltage:



- Both show that the potential of terminal a is 9V higher than the potential of terminal b.

17

## 1.6 Power and Energy


- Power is the time rate of expending or absorbing energy, measured in watts (W).

- Mathematical expression:

$$p = \frac{dw}{dt} = \frac{dw}{dq} \cdot \frac{dq}{dt} = vi \quad 1.3$$


ปกติเรากำหนดให้กระแสไหล  
จากแรงดันบวกไปแรงดันลบ

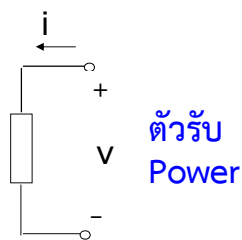ถ้ากระแสไหลจากแรงดันลบ  
ไปแรงดันบวก แสดงว่า  
กระแสมีค่าติดลบ



$P = +vi$   
absorbing power

Passive sign convention

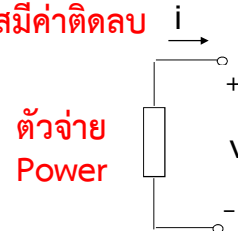


$p = -vi$   
supplying power

18

## 1.6 Power and Energy
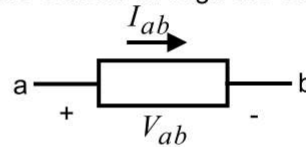
### Passive Sign Convention

- For calculating absorbed power: The power absorbed by any circuit element with terminals A and B is equal to the voltage drop from A to B multiplied by the current through the element from A to B, i.e.,  $P = V_{ab} \times I_{ab}$




- With this convention if  $P \geq 0$ , then the element is absorbing (consuming) power. Otherwise (i.e.,  $P < 0$ ) is absorbing negative power or actually generating (delivering) power.

19

## 1.6 Power and Energy
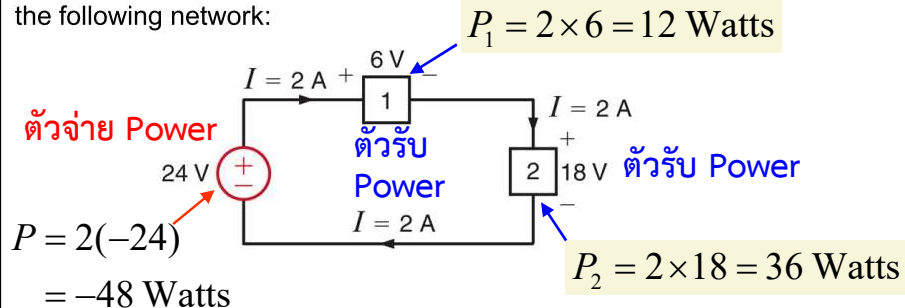
### Exercise

Determine the power absorbed or supplied by the elements of the following network:



Passive sign convention is satisfied when the current enters through the positive terminal of an element and  $p = +vi$ . If the current enters through the negative terminal,  $p = -vi$ .

20

## 1.6 Power and Energy

- The law of conservation of energy must be obeyed in any electric circuit. For this reason, the algebraic sum of power in a circuit, at any instant of time, must be zero

$$\sum p = 0$$

- Energy is the capacity to do work, measured in joules (J).
- Mathematical expression  $w = \int_{t_0}^t p dt = \int_{t_0}^t v i dt$  1.4

21

## Side note

### The Three Laws of Thermodynamics

The first law, also known as Law of Conservation of Energy, states that energy cannot be created or destroyed in an isolated system.

The second law of thermodynamics states that the entropy of any isolated system always increases.

The third law of thermodynamics states that the entropy of a system approaches a constant value as the temperature approaches absolute zero.

src: <https://courses.lumenlearning.com/introchem/chapter/the-three-laws-of-thermodynamics>

22

## 1.6 Power and Energy

### Tellegan's Theorem

- **Principle of Conservation of the Power:** The algebraic sum of the powers absorbed by all elements in a circuit is zero at any instance of time ( $\sum P=0$ ). That is, the sum of absorbed powers is equal to the sum of generated powers at each instance of time.
- This principle is also known as Tellegan's theorem. (Bernard D.H. Tellegan (1900-1990), a Dutch electrical engineer)



- Similarly, one can write the principle of conservation of energy.

23

### Example 3 Power, Energy, and the Passive Convention

Consider the circuit shown in Figure 1.5-4 with  $v(t) = 12e^{-8t}$  V and  $i(t) = 5e^{-8t}$  A for  $t \geq 0$ . Both  $v(t)$  and  $i(t)$  are zero for  $t < 0$ . Find the power supplied by this element and the energy supplied by the element over the first 100 ms of operation.



FIGURE 1.5-4 The element considered in Example 1.5-3.

#### Solution

The power

$$p(t) = v(t) i(t) = (12e^{-8t})(5e^{-8t}) = 60e^{-16t} \text{ W}$$

is the power *supplied* by the element because  $v(t)$  and  $i(t)$  do not adhere to the passive convention. This element is supplying power to the charge flowing through it.

The energy supplied during the first 100 ms = 0.1 seconds is

$$\begin{aligned} w(0.1) &= \int_0^{0.1} p \, dt = \int_0^{0.1} (60e^{-16t}) \, dt \\ &= 60 \left. \frac{e^{-16t}}{-16} \right|_0^{0.1} = -\frac{60}{16} (e^{-1.6} - 1) = 3.75(1 - e^{-1.6}) = 2.99 \text{ J} \end{aligned}$$

24

## 1.7 Circuit Elements

### Circuit Elements


- Circuit components can be broadly classified as being either **active** or **passive**.
- An active element is capable of generating energy.
  - Example: current or voltage sources
- A passive element is an element that does not generate energy, however, they can either consume or store energy.
  - Example: resistors, capacitors, and inductors

25

## 1.7 Circuit Elements

### Active Elements

### Passive Elements

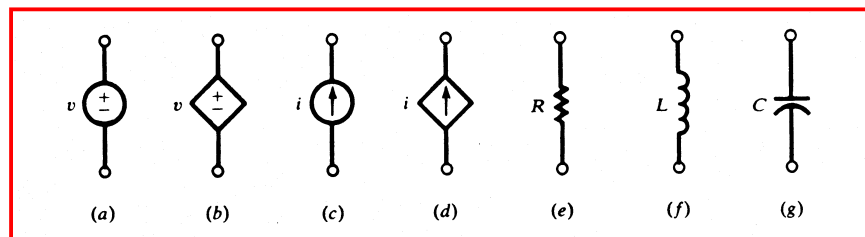


Independent sources      Dependent sources

- A dependent source is an active element in which the source quantity is controlled by another voltage or current.
- They have four different types: VCVS, CCVS, VCCS, CCCS. Keep in mind the signs of dependent sources.


26
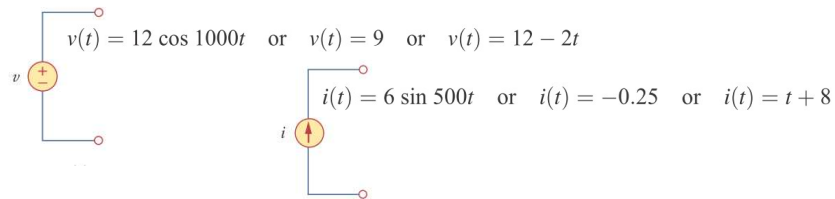
## 1.7 Circuit Elements

An **ideal independent source** is an active element that provides a specified voltage or current that is completely independent of other circuit elements.



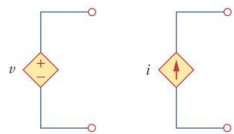An **ideal dependent (or controlled) source** is an active element in which the source quantity is controlled by another voltage or current.




1. A voltage-controlled voltage source (VCVS).
2. A current-controlled voltage source (CCVS).
3. A voltage-controlled current source (VCCS).
4. A current-controlled current source (CCCS).

27


## 1.7 Circuit Elements
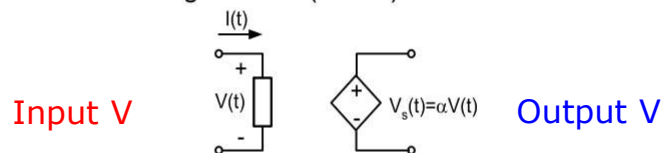
### Dependent (Controlled) Source

- There are four types of dependent sources:
- Voltage-controlled voltage source (VCVS)



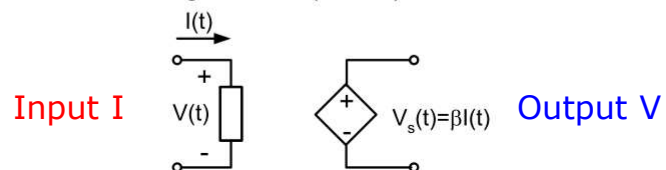- Current-controlled voltage source (CCVS)




28


## 1.7 Circuit Elements
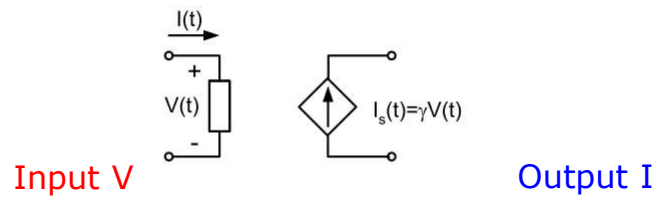
### Dependent (Controlled) Source

- Voltage-controlled current source (VCCS)



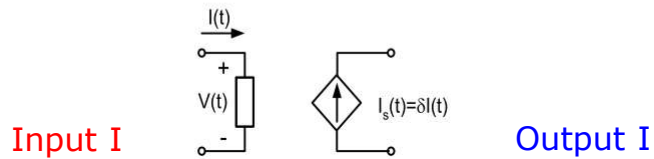- Current-controlled current source (CCCS)




29

## 1.7 Circuit Elements


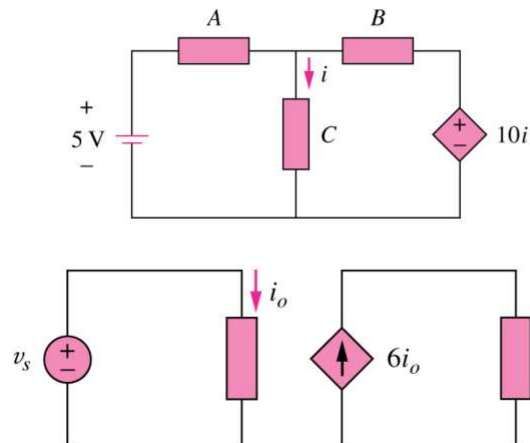
### Exercise

In the following circuits, identify the type of dependent sources:




30

## 1.7 Circuit Elements

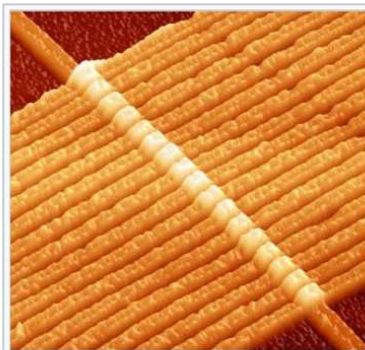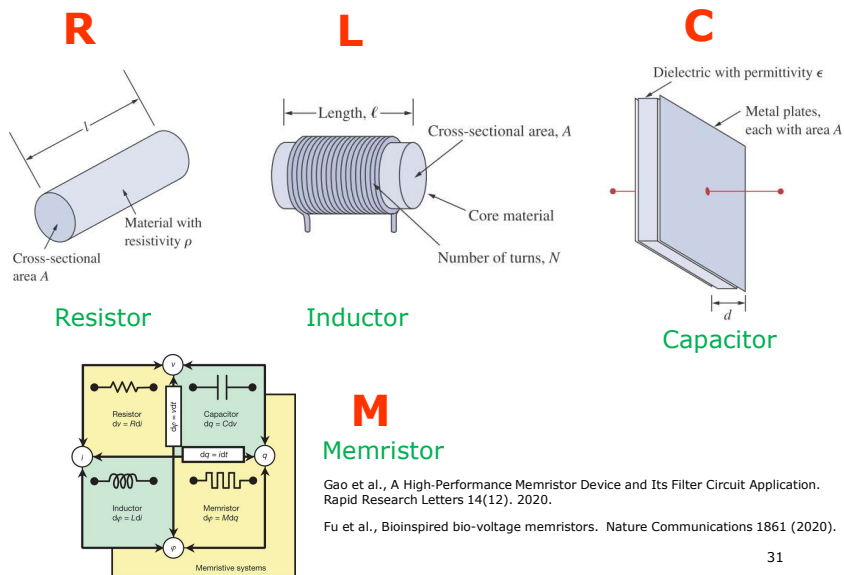

An array of 17 purpose-built oxygen-depleted titanium dioxide memristors built at HP Labs, imaged by an atomic force microscope. The wires are about 50 nm, or 150 atoms, wide.<sup>[20]</sup> Electric current through the memristors shifts the oxygen vacancies, causing a gradual and persistent change in electrical resistance.<sup>[21]</sup>

## Memristor

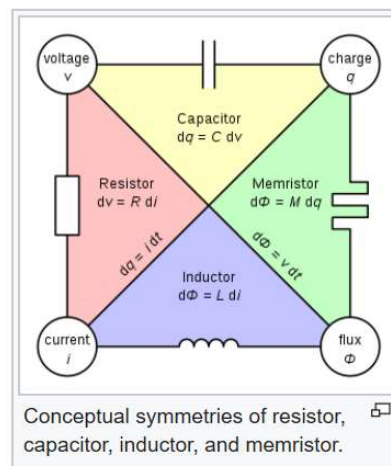



## 1.7 Circuit Elements

### **Example 4**

Obtain the voltage  $v$  in the branch shown in Figure 2.1.1P for  $i_2 = 1\text{ A}$ .

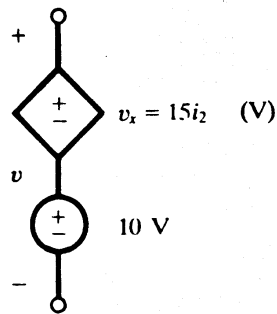


Figure 2.1.1P

33

## 1.7 Circuit Elements

### **Solution**

Voltage  $v$  is the sum of the current-independent 10-V source and the current-dependent voltage source  $v_x$ .

Note that the factor 15 multiplying the control current carries the units  $\Omega$ .

$$\text{Therefore, } v = 10 + v_x = 10 + 15(1) = 25 \text{ V}$$

34